

Review of Biomedical Instrumentation



COLUMBIA | ENGINEERING
The Fu Foundation School of Engineering and Applied Science




Module final: Nov. 5, 2025

- You can bring:
 - The Laplace transform table (with no notes)
 - A simple calculator with trigonometric functions
 - Smart phone **NOT** allowed
 - Cheat-sheet **NOT** allowed
- Office hours
 - Oct. 30 (Thursday): 11-1pm, BME multi-purpose room Mudd 343
 - Nov. 4 (Tuesday): 10-12pm, BME conference room ET353

Biomedical instrumentation


- Multiple stages

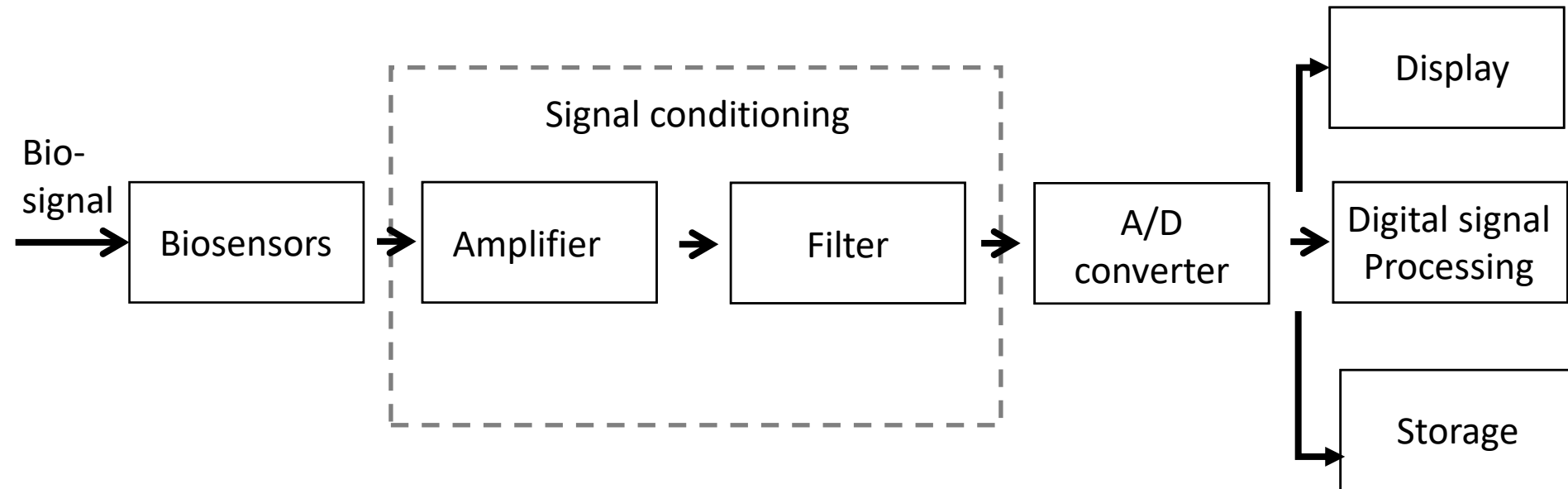



Accuracy & precision

- Accuracy refers to the difference between the true value and the actual value measured by the sensor.
- Precision refers to the degree of measurement reproducibility


Not Accurate or Precise

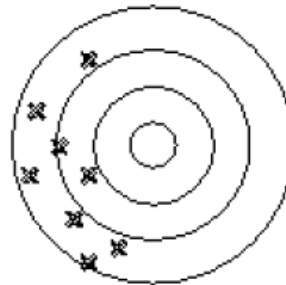

Precise and NOT Accurate

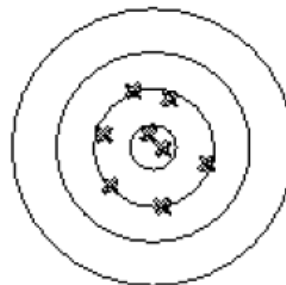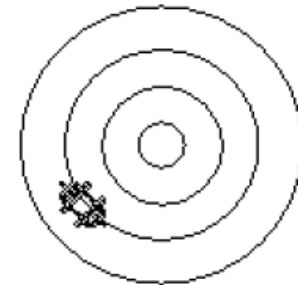

Accurate and NOT Precise

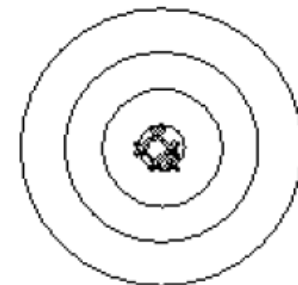


Precise and Accurate

Variable-resistive sensors

- The resistance of an electrical conductor is

$$R = \frac{\rho L}{A}$$

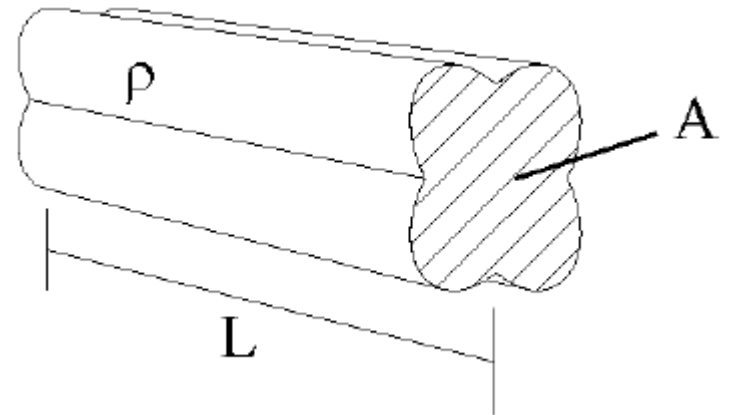

Where:

R is resistance

L is the length of the conductor

A is the cross-sectional area of the conductor

P is the resistivity of the material

Strain gages

- One of the most common displacement transducer (strain -> change in resistance)
- Strain, or axial strain, is defined as the fractional change in length in response to applied force:

$$\varepsilon = \frac{\Delta L}{L}$$

Strain gages

- What the relationship between ΔR and ϵ ?

$$dR = d\left(\frac{\rho L}{A}\right) = \frac{\rho}{A} dL + \frac{L}{A} d\rho - \frac{\rho L}{A^2} dA$$



$$\frac{dR}{R} = \frac{dL}{L} + \frac{d\rho}{\rho} - \frac{dA}{A}$$

Strain gages

- Poisson's ratio defines the relationship between the change in diameter of a body experiencing uniaxial stress and change in length

$$\nu = -\frac{\Delta D}{D} / \frac{\Delta L}{L}$$

Minus sign means increase in diameter resulting in decrease in length

Strain gages

- For a circular wire, the cross-sectional area

$$A = \pi \left(\frac{D}{2} \right)^2$$

$$\Delta A = d \left(\pi \left(\frac{D}{2} \right)^2 \right) = \pi \left(\frac{D}{2} \right) dD$$


$$\frac{\Delta A}{A} = -2\nu \frac{\Delta L}{L}$$

Strain gages

$$\frac{\Delta R}{R} = (1 + 2\nu) \frac{\Delta L}{L} + \frac{\Delta \rho}{\rho}$$



Dimensional effect



Piezoresistive effect: changes in the lattice structure of the material induced by strain

Strain gages

- The gage factor G

$$G = \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} = (1 + 2\nu) + \frac{\frac{\Delta \rho}{\rho}}{\frac{\Delta L}{L}}$$


- The gage factor for most metals is primarily a function of dimensional effects, i.e. $G = (1 + 2\nu)$

$$\varepsilon = \frac{1}{G} \frac{\Delta R}{R}$$

Strain gages

- The strain and change in resistance

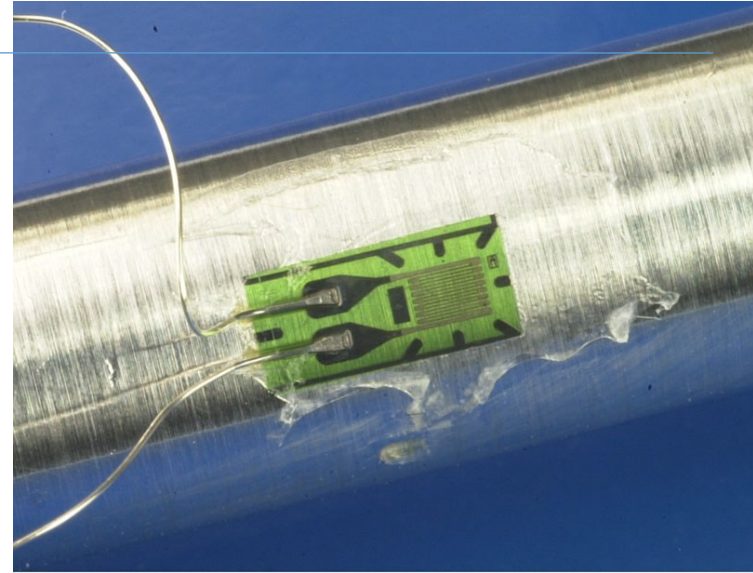
$$\varepsilon = \frac{\Delta L}{L} = \frac{1}{G} \frac{\Delta R}{R}$$



- Strain of material is typically very small
- A typical strain gage has $G = 2$, $R=300\Omega$, given a strain of 0.000001 , the change in resistance is

$$\Delta R = \varepsilon GR = 600\mu\Omega \quad \text{Too small to measure with a multimeter!}$$


Wheatstone Bridge

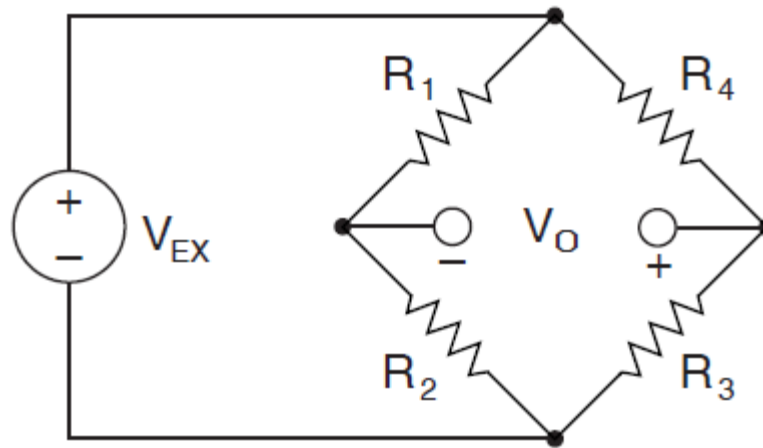

$$V_O = \left(\frac{R_3}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) V_{EX}$$

- If $R_4/R_3 = R_1/R_2$, the $V_O = 0$, which means the bridge is balanced.

Quarter Wheatstone Bridge


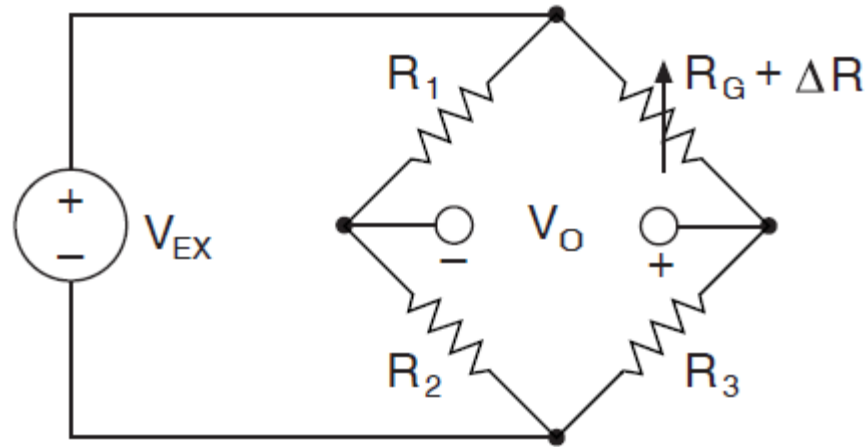


- If $R_1 = R_2$, and $R_3 = R_G$,

$$V_0 = -\frac{G \cdot \varepsilon}{4} \frac{1}{1 + \frac{G \cdot \varepsilon}{2}} V_{EX}$$



Where G is gage factor

Half Wheatstone Bridge

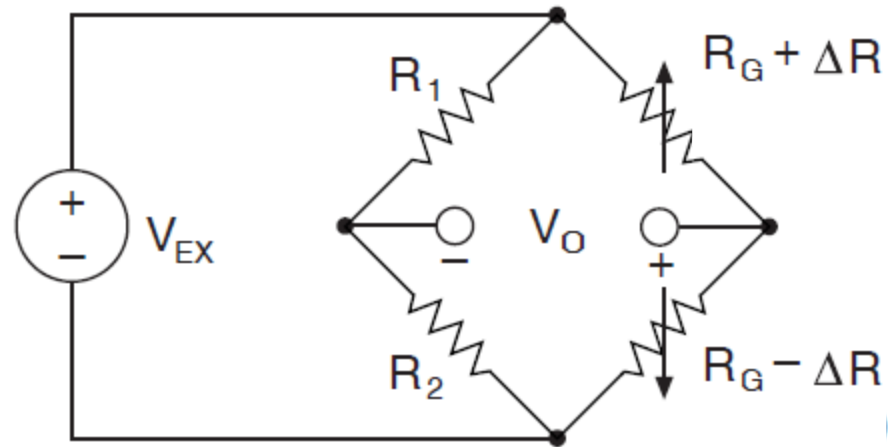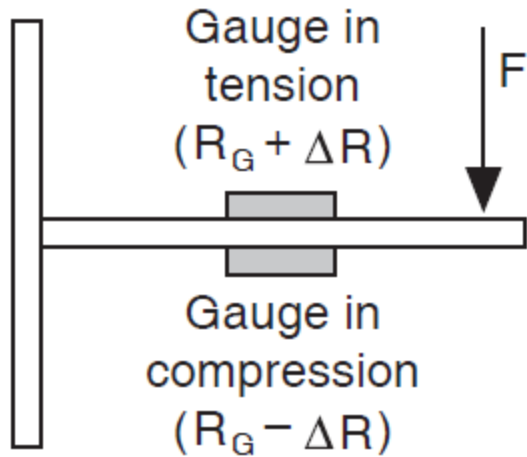


$$V_0 = -\frac{G \cdot \varepsilon}{2} V_{EX}$$

Full Wheatstone Bridge

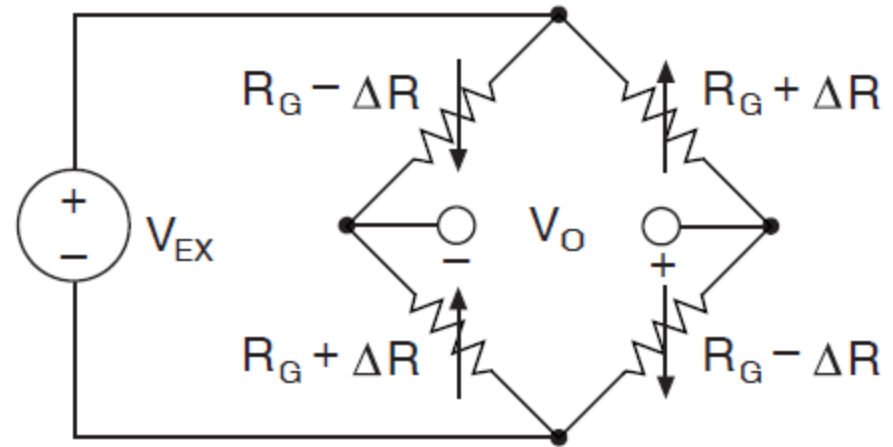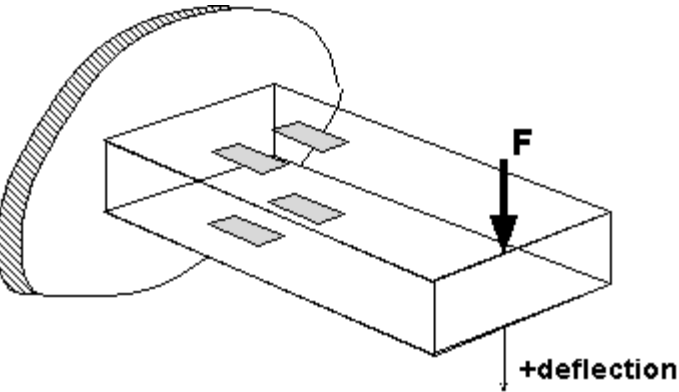

$$V_0 = -G \cdot \varepsilon \cdot V_{EX}$$

Circuit analysis in Laplace domain

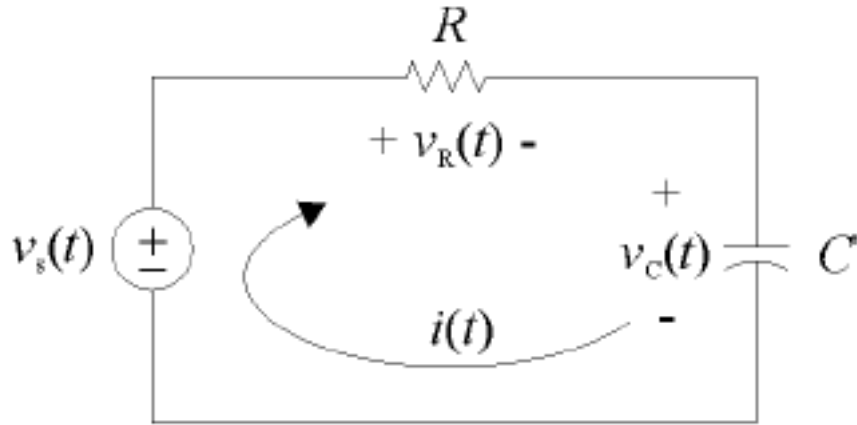

$$V_s(t) = RC \frac{dV_c(t)}{dt} + V_c(t)$$

$$V_s(t) = u(t)$$

Laplace transform

$$V_c(s) = \frac{1}{1 + RCs} \cdot \frac{1}{s}$$


Inverse Laplace transform

$$V_c(t) = 1 - e^{-\frac{t}{RC}}$$

Noise

- Any unwanted signal that corrupts the signal of interest.
- Common types of noise are:
 - Extraneous noise
 - Thermal noise (white noise)
 - power noise
 - $1/f$ noise (pink noise)

Low pass filter

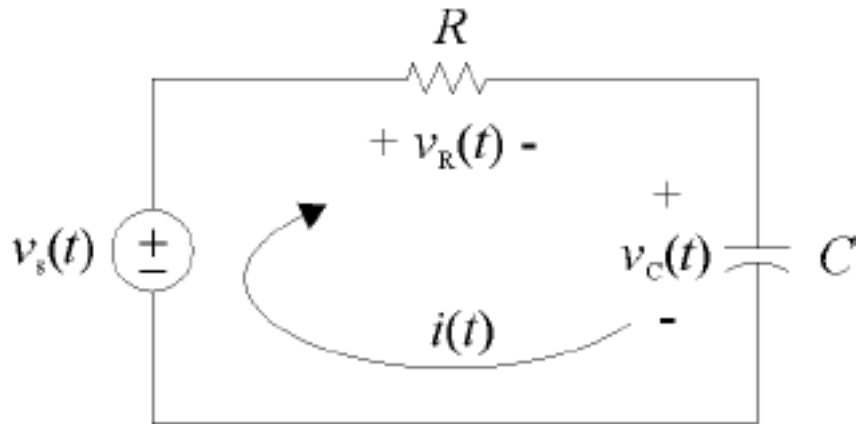

- Input signal:

$$v_s(t) = \sin(t) + \sin(100t)$$

- What is the voltage across the capacitor?

$$V_c(s) = \frac{1}{1 + RCs} V_s(s)$$

$$V_s(s) = \frac{1}{s^2 + 1} + \frac{100}{s^2 + 100^2}$$

Low-pass filter

$$V_c(s) = \frac{1}{1 + RCs} \cdot \frac{1}{s^2 + 1} + \frac{1}{1 + RCs} \cdot \frac{100}{s^2 + 100^2}$$

Response to sinusoidal input with a
freq. of 1 rad/s

Response to sinusoidal input with a
freq. of 100 rad/s

Low-pass filter

- Response to the 1 rad/s sinusoidal signal

$$V_{c1}(s) = \frac{1/RC}{s + 1/RC} \cdot \frac{1}{s^2 + 1}$$

$$L^{-1}[V_{c1}(s)] = \frac{1}{RC} \left(\frac{1}{\left(\frac{1}{RC}\right)^2 + 1} e^{-\frac{t}{RC}} + \frac{1}{\sqrt{\left(\frac{1}{RC}\right)^2 + 1}} \sin(t - \theta) \right)$$

$$= \frac{RC}{(RC)^2 + 1} e^{-\frac{t}{RC}} + \frac{1}{\sqrt{(RC)^2 + 1}} \sin(t - \theta)$$

Transient response

Steady-state response

Where: $\theta = \tan^{-1}(RC)$

Low-pass filter

- Response to the 100 rad/s sinusoidal signal

$$V_{c2}(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \cdot \frac{100}{s^2 + 100^2}$$

$$\begin{aligned} L^{-1}[V_{c2}(s)] &= \frac{1}{RC} \left(\frac{100}{\left(\frac{1}{RC}\right)^2 + 100^2} e^{-\frac{t}{RC}} + \frac{1}{\sqrt{\left(\frac{1}{RC}\right)^2 + 100^2}} \sin(100t - \theta) \right) \\ &= \frac{100RC}{(100RC)^2 + 1} e^{-\frac{t}{RC}} + \frac{1}{\sqrt{(100RC)^2 + 1}} \sin(100t - \theta) \end{aligned}$$

$$\text{Where: } \theta = \tan^{-1}(100RC)$$

Low-pass filter

$$v_s(t) = \sin(t) + \sin(100t)$$

- If $RC = 1$

$$V_{c1}(t) = \frac{1}{\sqrt{(RC)^2 + 1}} \sin(t - \theta) = \frac{1}{\sqrt{2}} \sin(t - \theta)$$

$$V_{c2}(t) = \frac{1}{\sqrt{(100RC)^2 + 1}} \sin(100t - \theta)$$

$$= \frac{1}{\sqrt{10001}} \sin(100t - \theta)$$

High frequency signal was attenuated by 99% while the low frequency signal was attenuated by 30%

Discrete Fourier Transform

- DFT is necessary to analyze and represent discrete signals in the frequency domain.

$$X(m) = \sum_{k=0}^{N-1} x(k) e^{-j \frac{2\pi mk}{N}}; m = 0, 1, \dots, N - 1$$

Where the index m represents the digital frequency index, $x(k)$ is the sampled data of $x(t)$, and N is an even number that represents the number of samples for $x(k)$

Fast Fourier Transform (FFT)

- DFT needs $O(N^2)$ operations because it has $N/2$ outputs X_k , and each output requires a sum of N terms
- If N is a power of 2, some tricks can be used compute the same result with only $(N/2)\log_2(N)$ operations. This is called Fast Fourier Transform, which is significantly faster.

Estimation issues

- The highest frequency that can be estimated is determined by the rate at which the signal was sampled and is given by

$$f_{\max} = \frac{1}{2T_s}$$

Where T_s is sampling interval

Estimation issues

- The frequency resolution of spectral estimates is also determined by the segment length and the sampling frequency


$$\Delta f = \frac{f_s}{N}$$

Where f_s is sampling frequency,
and N is the length of data

Estimation issues


- As with the Fourier transform, record length selection is particularly important when computing the spectra of periodic signals; it is best to choose a record length that yields a frequency increment that divides evenly into the signal's fundamental frequency.
- For FFT, since the number of samples must be a power of 2, it sometimes may lead to estimates at strange frequencies.

Wagon-wheel effect

 

Aliasing

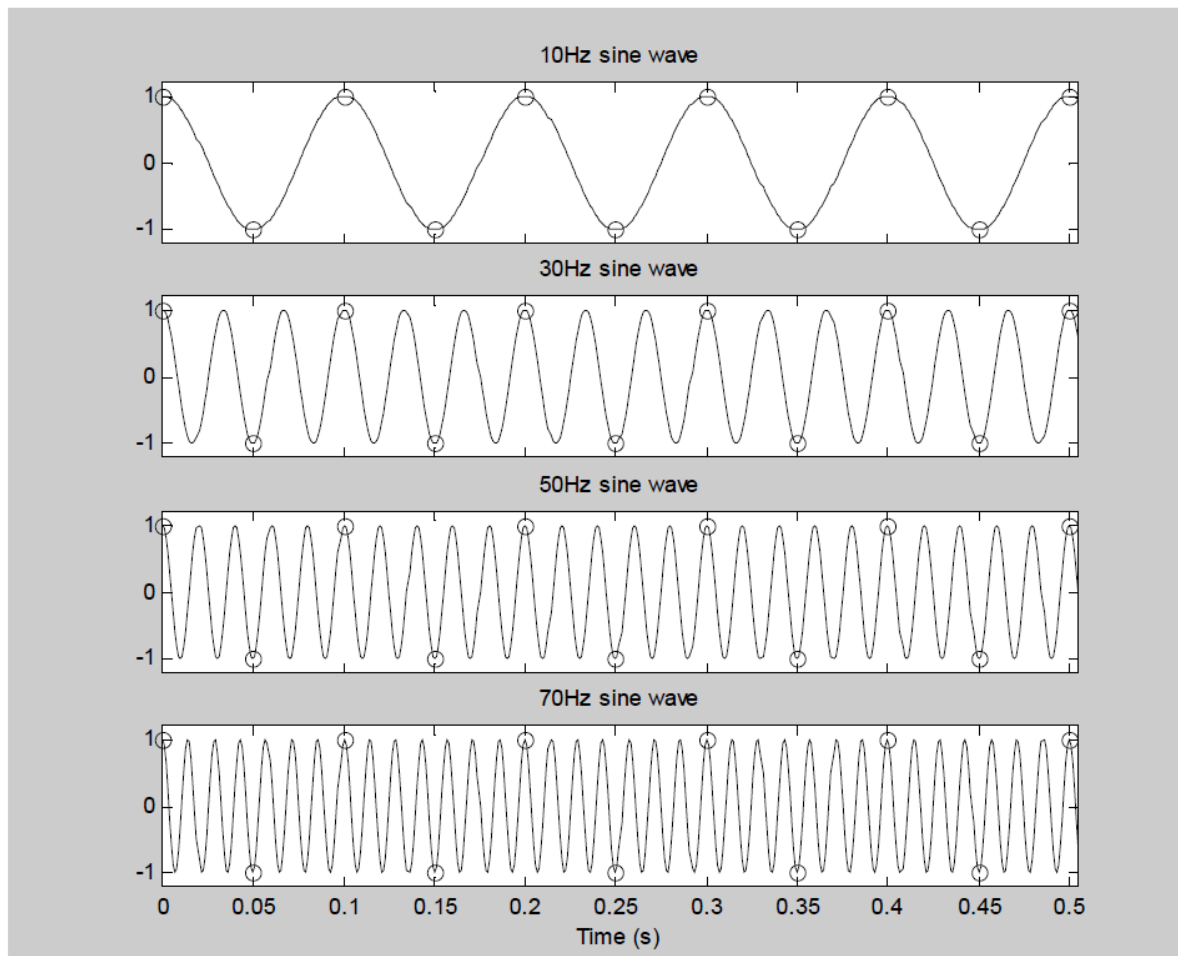- Aliasing is the confusion of high- and low-frequency components in the original (analog) signal



Aliasing

- For a signal sampled at a rate of f_s samples/second, the frequencies given by

$$f_i = nf_s \pm f \text{ for } n = 1, 2, 3, \dots$$

$$\text{where } 0 \leq f \leq \frac{f_s}{2}$$

cannot be distinguished from each other.

Aliasing

- With a sampling rate of 20 Hz, components with frequencies of 10, 30, 50, 70, etc. will all yield exactly the same sample values, since they are aliased to 10 Hz.

