

ELEN E3401: Electromagnetics

Spring 2025

Prof. Keren Bergman


Lecture #5



COLUMBIA | ENGINEERING
The Fu Foundation School of Engineering and Applied Science



Traveling wave solutions

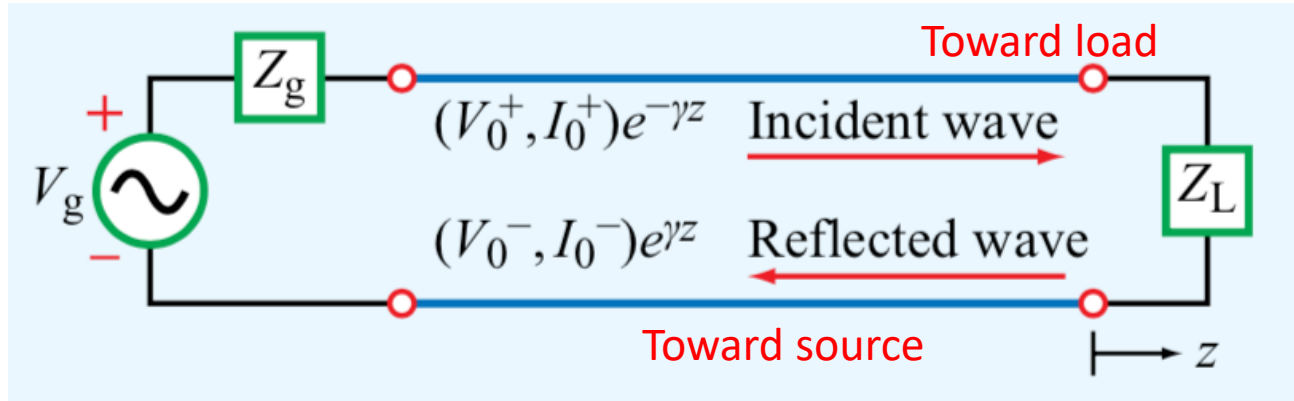

4 unknowns:
 (V_0^+, I_0^+) and (V_0^-, I_0^-)

Wave amplitudes of
 incident/reflected

Relate the 4 wave amplitudes: I_0^+ and I_0^- to V_0^+ and V_0^-

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad \text{Total voltage}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad \text{Total current}$$

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L')\tilde{I}(z) \leftarrow \text{Transmission line voltage phasor equation}$$

$$-\frac{d\tilde{V}(z)}{dz} = \gamma V_0^+ e^{-\gamma z} - \gamma V_0^- e^{\gamma z} = (R' + j\omega L')\tilde{I}(z)$$

$$\Rightarrow \tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}].$$

Characteristic Impedance

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad \tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}]$$

$$I_0^+ = \frac{V_0^+ \gamma}{(R' + j\omega L')} \quad \text{and} \quad I_0^- = \frac{-V_0^- \gamma}{(R' + j\omega L')}$$

Define the ratio: $\frac{V_0^+}{I_0^+} = Z_0 = \frac{-V_0^-}{I_0^-}$

- Z_0 is the characteristic impedance
- Z_0 is the ratio of voltage amplitude to current amplitude for each individual traveling wave
- *Not* ratio of total $\tilde{V}(z)$ and $\tilde{I}(z)$

Characteristic impedance

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad \Omega$$

Wave Propagation in Transmission Line

Voltage \sim related to \vec{E} , current \sim related to \vec{H}

$$\frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-}$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}$$

$$\left\{ \begin{array}{l} Z_0 : \text{characteristic impedance} \rightarrow \omega \text{ and } R', L', G', C' \\ \tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \\ \tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \end{array} \right.$$

2 equations, 2 unknowns

Wave Propagation in Transmission Line

$$V_0^+ = |V_0^+|e^{j\varphi^+}$$

$$V_0^- = |V_0^-|e^{j\varphi^-}$$

We will apply boundary conditions at the source and load to obtain values for V_0^+ and V_0^-

Now can convert back to time domain:

$$v(z, t) = \text{Re}\{[\tilde{V}(z)]e^{j\omega t}\}$$

$$= \text{Re}[(V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z})e^{j\omega t}]$$

$$= \text{Re}[|V_0^+|e^{j\varphi^+} e^{j\omega t} e^{-(\alpha+j\beta)z} + |V_0^-|e^{j\varphi^-} e^{j\omega t} e^{(\alpha+j\beta)z}]$$

$$v(z, t) = |V_0^+|e^{-\alpha z} \cos(\omega t - \beta z + \varphi^+) \quad \longleftarrow \quad +z \text{ direction} \\ + |V_0^-|e^{\alpha z} \cos(\omega t + \beta z + \varphi^-) \quad \longleftarrow \quad -z \text{ direction}$$

Wave Propagation in Transmission Line

Both +z and -z propagating waves have same phase velocity:

$$u_p = f\lambda = \frac{\omega}{\beta} .$$

↑
Guided wavelength

$e^{-\alpha z} \rightarrow$ attenuation for +z

$e^{\alpha z} \rightarrow$ attenuation for -z

Standing Wave:

- Lossless TL: $\alpha = 0$
- Lossy TL: $\alpha \neq 0$

TL Wave Propagation - Summary

We obtained:

$$\left\{ \begin{array}{l} \tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \quad \text{where } Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \end{array} \right.$$

In general:

$$\left\{ \begin{array}{l} V_0^+ = |V_0^+| e^{j\varphi^+} \\ V_0^- = |V_0^-| e^{j\varphi^-} \end{array} \right.$$

And the time domain, instantaneous solution:

$$v(z, t) = |V_0^+| e^{-\alpha z} \underbrace{\cos(\omega t - \beta z + \varphi^+)}_{+z \text{ wave}} + |V_0^-| e^{\alpha z} \underbrace{\cos(\omega t + \beta z + \varphi^-)}_{-z \text{ wave}}$$

Standing wave

$$u_p = f\lambda = \frac{\omega}{\beta}$$


$e^{-\alpha z} \rightarrow \text{attenuation}$

Lossless TL: $\alpha = 0$

Lossless Transmission Line

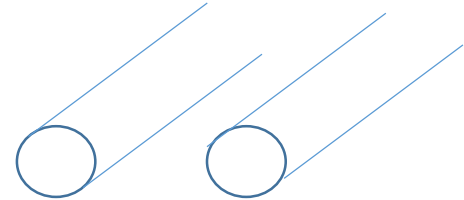Example: air line

Air separates 2 conductors $\rightarrow G'=0$ because $\sigma = 0$
Also, assume high conductivity, and $R'=0$



Consider air line:

$$Z_0 = 50\Omega$$

Phase constant = **20 rad/m** at **f = 700 MHz**

Q: Find L' and C' of the transmission line.

Lossless Transmission Line

Q: Find L' and C' of the air transmission line ($G'=0$, $R'=0$)

- $Z_0 = 50\Omega$
- $\beta = 20 \text{ rad/m}$
- $f = 700 \text{ MHz}$

Solution:

$$\beta = \text{Im}(\gamma) = \text{Im}\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) = \text{Im}(j\omega\sqrt{L'C'}) = \omega\sqrt{L'C'}$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}} \quad \rightarrow \quad \omega C' = \frac{\beta}{Z_0}$$


$$C' = \frac{\beta}{\omega Z_0} = 90.9 \text{ pF/m}$$

$$Z_0 = \sqrt{\frac{L'}{C'}} \rightarrow L' = 227 \text{ nH/m}$$

TL Wave Propagation - Summary

We obtained: $\left\{ \begin{array}{l} \tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \end{array} \right.$

In general: $\left\{ \begin{array}{l} V_0^+ = |V_0^+| e^{j\varphi^+} \\ V_0^- = |V_0^-| e^{j\varphi^-} \end{array} \right.$

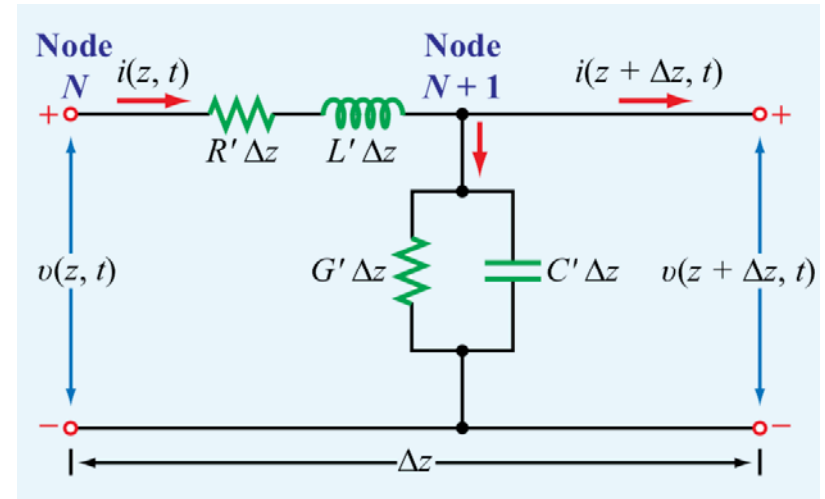

$$\text{where } Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

And the time domain, instantaneous solution:

$$v(z, t) = |V_0^+| e^{-\alpha z} \underbrace{\cos(\omega t - \beta z + \varphi^+)}_{\text{+z wave}} + |V_0^-| e^{\alpha z} \underbrace{\cos(\omega t + \beta z + \varphi^-)}_{\text{-z wave}}$$

Lossless transmission line

Consider a lossless line, $\gamma = j\beta$

$$\tilde{V}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$\tilde{I}(z) = I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z}$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

Recall these were solutions to wave equations:

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0$$


$$\frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0$$

$V_0^+ e^{-j\beta z} \rightarrow$ incident wave travels +z (source \rightarrow load)

$V_0^- e^{j\beta z} \rightarrow$ reflected wave travels -z (load \rightarrow source)

Full circuit with transmission line

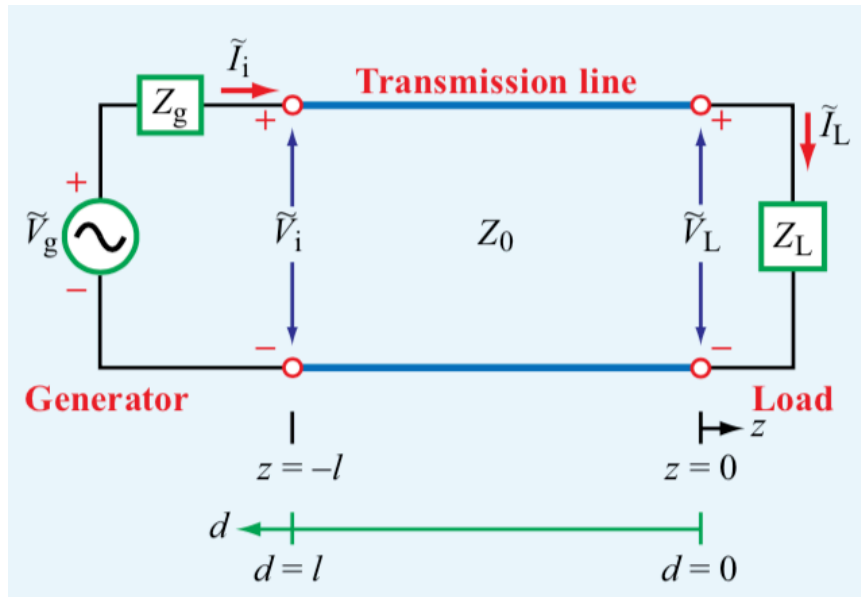Consider full circuit with TL, generator and load impedance Z_L ($z = 0$ at load)



“ z ” points from generator to load

“ d ” is distance from load $d = -z$


Generator at $z = -l$, $d = l$, $d = -z$

Load at $z = 0$, $d = 0$

At sending end, $z = -l$

connected to sinusoidal voltage source: \tilde{V}_g and internal impedance Z_g

Voltage Reflection Coefficient

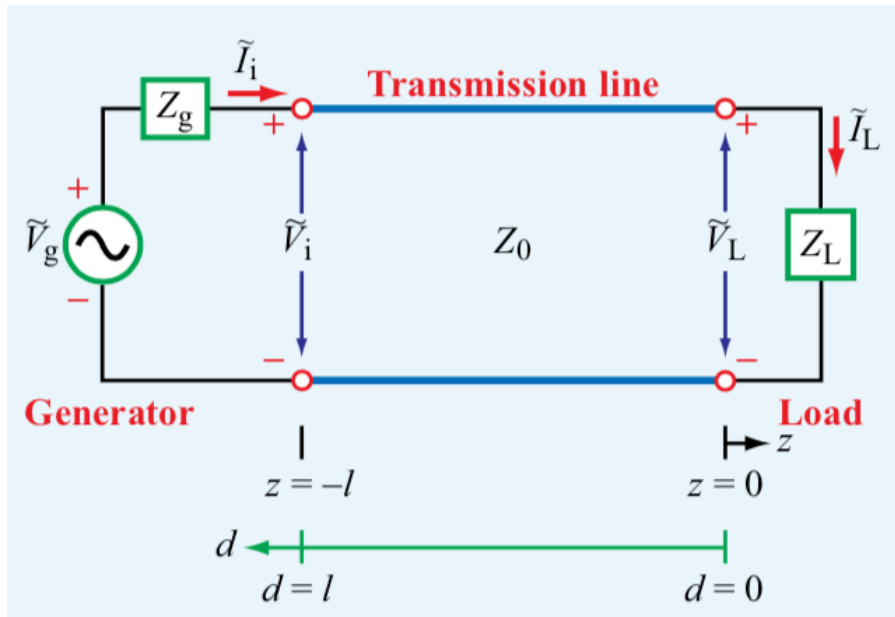

“ z ” points from generator to load

“ d ” is distance from load $d = -z$

At the load, \tilde{V}_L = phasor voltage across load
 \tilde{I}_L = phasor current through load

$$\text{load impedance} = Z_L = \frac{\tilde{V}_L}{\tilde{I}_L}$$


\tilde{V}_L , \tilde{I}_L are total voltage, current at $z = 0$ (at load)

Voltage Reflection Coefficient

$$\tilde{V}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$\tilde{I}(z) = I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z}$$
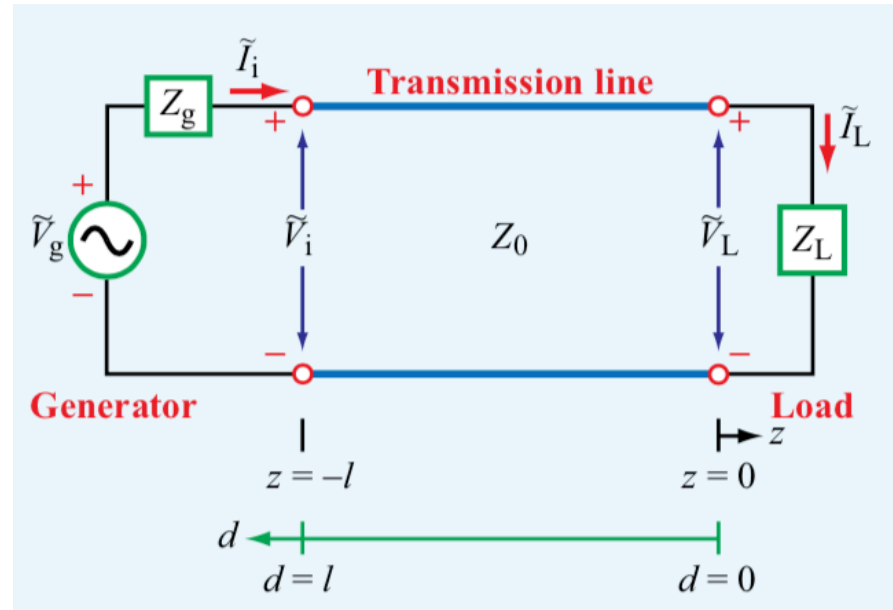
$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$



At the load, $z = 0$:

$$\tilde{V}_L = \tilde{V}(z = 0) = V_0^+ + V_0^-$$


$$\tilde{I}_L = \tilde{I}(z = 0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

$$Z_L = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0 \quad \text{Load impedance}$$

$$V_0^- = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) V_0^+$$

Solve for V_0^+ , V_0^-

Voltage Reflection Coefficient

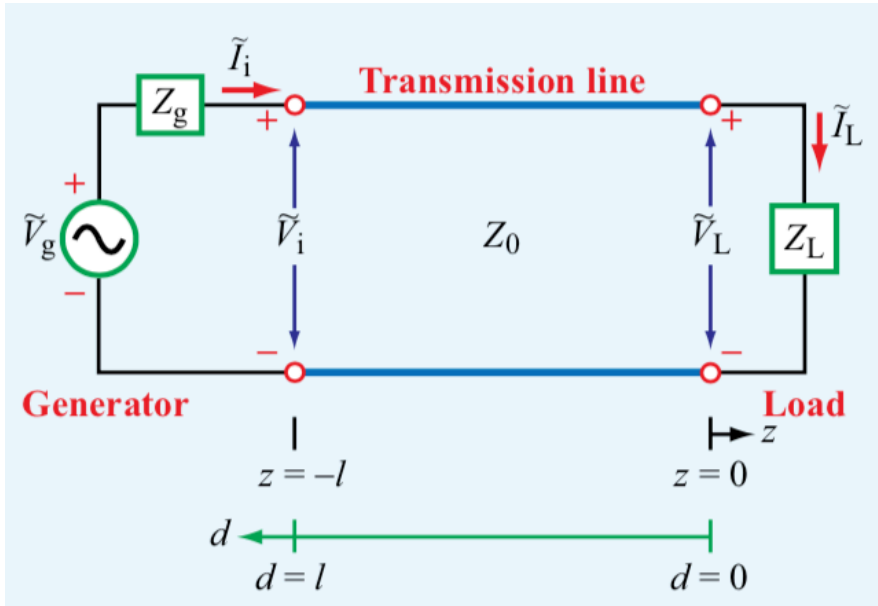

At the load, $z = 0$:

$$\tilde{V}_L = \tilde{V}(z = 0) = V_0^+ + V_0^-$$

$$\tilde{I}_L = \tilde{I}(z = 0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

$$Z_L = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0 \quad \text{Load impedance}$$

$$V_0^- = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) V_0^+$$

Define the reflection coefficient for the voltage:

$$\Gamma = \frac{V_0^-}{V_0^+} \quad \left(\begin{matrix} ref \\ inc \end{matrix} \right) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{z_L - 1}{z_L + 1} \quad (z_L = \frac{Z_L}{Z_0})$$

small z_L = normalized load impedance
Load impedance normalized to
characteristic impedance

Voltage Reflection Coefficient

$$\frac{V_0^-}{V_0^+} = \Gamma \quad \frac{I_0^-}{I_0^+} = -\Gamma \quad z_L = \frac{Z_L}{Z_0}$$

$Z_0 = \underline{\text{real}}$ for lossless but $Z_L = R + j\omega L$ in general is complex

↑
example

$$\Gamma = |\Gamma|e^{j\theta r} \longleftarrow \Gamma \text{ complex } (|\Gamma| \leq 1)$$

1. Load is matched when $Z_L = Z_0$, then $\Gamma = 0$ and $V_0^- = 0$ (no reflection by load)
2. Load is open circuit when $Z_L = \infty$, then $\Gamma = 1$ and $V_0^- = V_0^+$ (reflection in phase, $\theta r = 0$)
3. Load is short circuit when $Z_L = 0$, then $\Gamma = -1$ and $V_0^- = -V_0^+$ (reflection out of phase $\theta r = \pm 180^\circ$)

Example – Reflection of series RC load


Consider a 100Ω transmission line, $Z_0 = 100\Omega$

Connected to load: resistor 50Ω in series with 10 pF capacitor:

$$R_L = 50\Omega,$$


$$C_L = 10\text{pF} = 10^{-11}\text{ F}$$

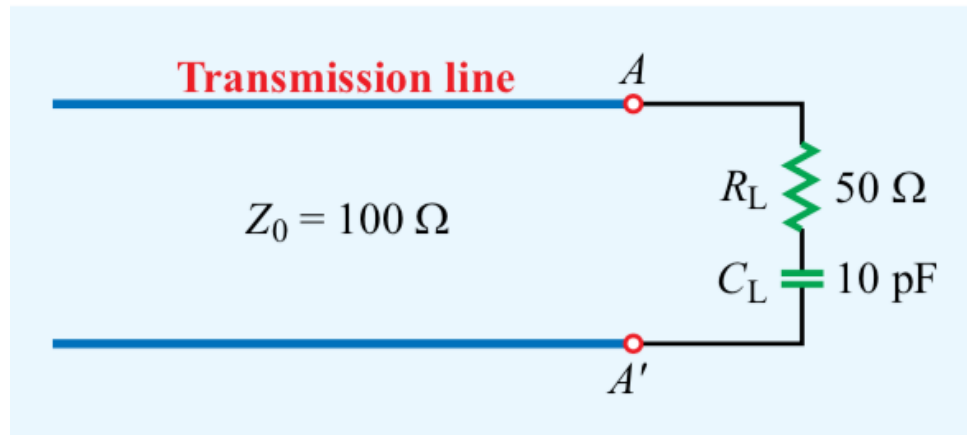Q: Find reflection coefficient for 100 MHz signal



$$f = 100\text{ MHz} = 10^8\text{ Hz}$$

Example – Reflection of series RC load

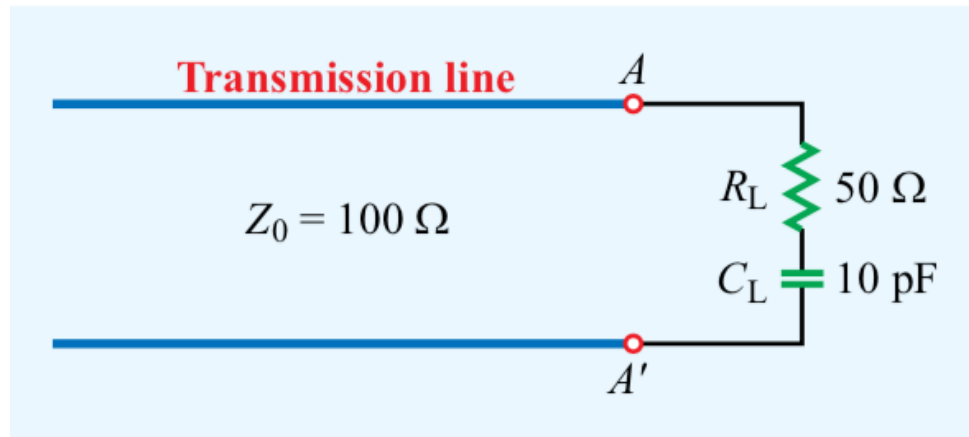

$$f = 100 \text{ MHz} = 10^8 \text{ Hz}$$

Solution: need to find Γ


$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{z_L - 1}{z_L + 1}$$

Find normalized impedance: $z_L = \frac{Z_L}{Z_0}$

$$z_L = \frac{Z_L}{Z_0} = \frac{R_L - j/(\omega C_L)}{Z_0} \quad (\text{Note: } R + \frac{1}{j\omega C} \rightarrow R - \frac{j}{\omega C})$$

$$= \frac{1}{100} \left(50 - j \frac{1}{2\pi \times 10^8 \times 10^{-11}} \right) = (0.5 - j1.59)\Omega$$

Example – Reflection of series RC load

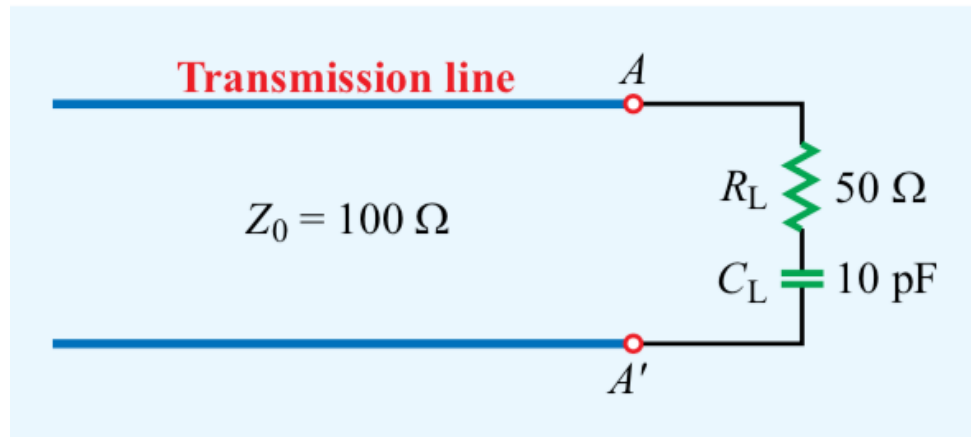

$$f = 100 \text{ MHz} = 10^8 \text{ Hz}$$

Solution:

Find the reflection coefficient (for voltage)

$$\Gamma = \frac{z_L - 1}{z_L + 1} = \frac{0.5 - j1.59 - 1}{0.5 - j1.59 + 1} = \frac{-0.5 - j1.59}{1.5 - j1.59} = \frac{-1.67e^{j72.6^\circ}}{2.19e^{-j46.7^\circ}}$$






$$\Gamma = -0.76 e^{j119.3^\circ} \quad (\text{Note: } -1 = e^{-j180^\circ})$$

$$\Gamma = e^{-j180^\circ} e^{j119.3^\circ} (0.76) = 0.76 \angle -60.7^\circ$$


\uparrow
 $|\Gamma|$

\uparrow
 θ_r

Reflection Coefficient $\Gamma = |\Gamma|e^{j\theta_r}$

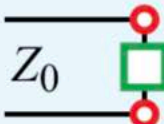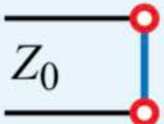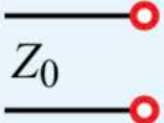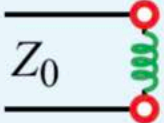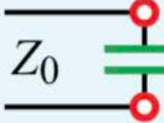Load	$ \Gamma $	θ_r
 Z_0 (Matched Load)	0 (no reflection)	irrelevant
 Z_0 (short)	1	$\pm 180^\circ$ (phase opposition)
 Z_0 (open)	1	0 (in-phase)
 $jX = j\omega L$ (Inductive Load)	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $jX = \frac{-j}{\omega C}$ (Capacitive Load)	1	$\pm 180^\circ + 2 \tan^{-1} x$

Microstrip Line


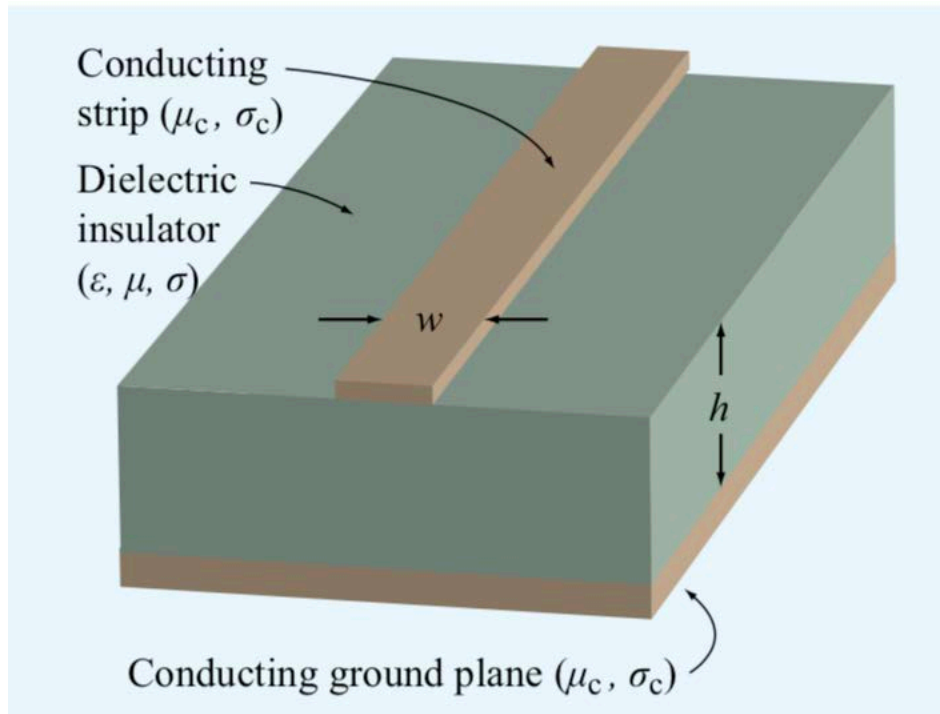


- Used in RF and microwave (high frequency) circuits
- Can fabricate on PCB

Geometric parameters:

- w = width
- h = thickness of dielectric
- We ignore strip thickness as long as $\ll w$

Microstrip Line

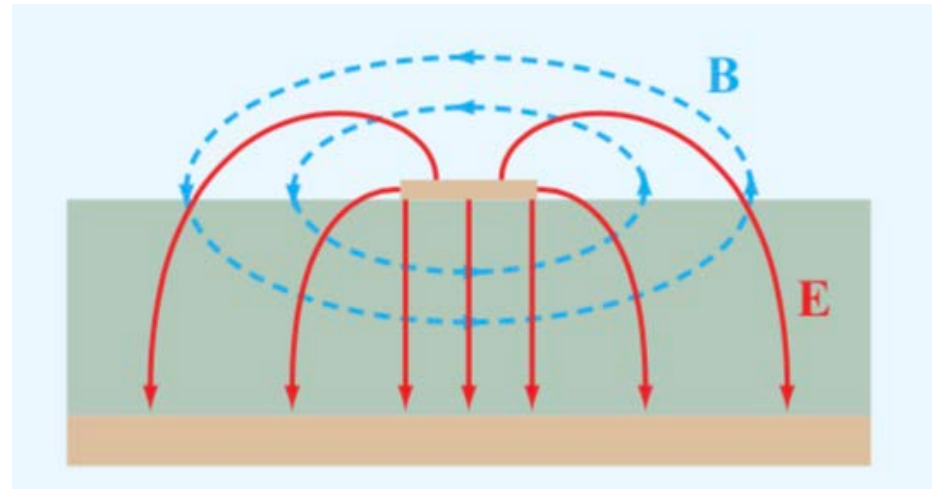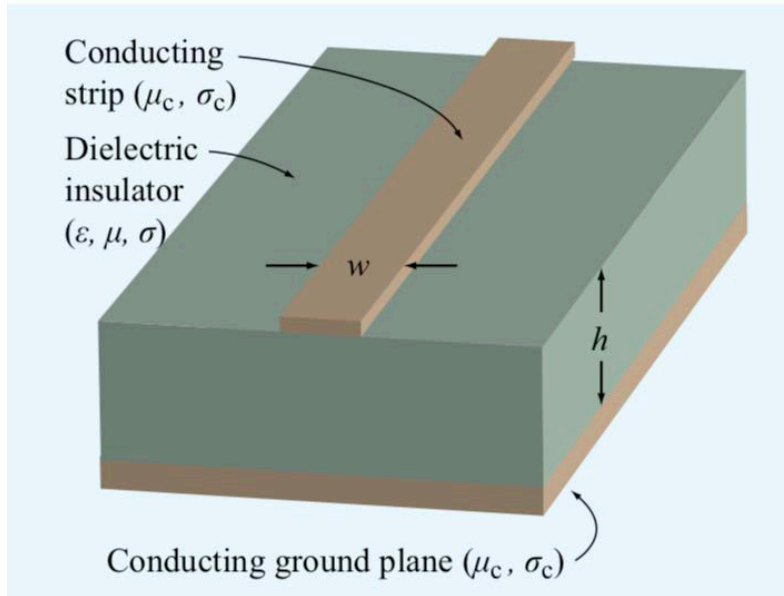

Region between conductors have approximately $\vec{E} \perp \vec{B}$
Quasi-TEM \rightarrow will model as TEM

Substrate = perfect dielectric, $\sigma = 0$

Metal strip / ground conductors = perfect conductors, $\sigma \rightarrow \infty$

Also, $\mu = \mu_0$

Microstrip Line

The key parameters become: w , h , ϵ

If \vec{E} is confined between conductors:

$$u_p = \frac{\omega}{\beta} = \frac{c}{\sqrt{\epsilon_r}} \quad \beta = \frac{\omega}{c} \sqrt{\epsilon_r}$$

where ϵ_r = relative permittivity of dielectric

Since some \vec{E} is through air, we define: ϵ_{eff} = effective permittivity

$$u_p = \frac{c}{\sqrt{\epsilon_{\text{eff}}}}$$

With significant derivation:

$$\epsilon_{\text{eff}} = \frac{\epsilon_r + 1}{2} + \left(\frac{\epsilon_r - 1}{2} \right) \left(1 + \frac{10}{s} \right)^{-xy}$$

where $s = \frac{w}{h}$ (width to thickness ratio)

Microstrip Line

From previous slide:

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \left(\frac{\epsilon_r - 1}{2} \right) \left(1 + \frac{10}{s} \right)^{-xy}$$

$x, y \rightarrow$ additional variables \rightarrow used to obtain:

Characteristic Impedance \rightarrow

$$Z_0 = \frac{60}{\sqrt{\epsilon_{eff}}} \ln \left\{ \frac{6 + (2\pi - 6)e^{-t}}{s} + \sqrt{1 + \frac{4}{s^2}} \right\}$$
$$t = \left(\frac{30.67}{s} \right)^{0.75}$$

Generalized, Lossless Transmission Line

Transmission line can be characterized by:

- Propagation constant: γ
 - Characteristic impedance: Z_0
- Then can specify ω , R' , L' , G' , C'

Want TL with low ohmic loss → get high σ_c conductors and dielectrics with $\sigma \rightarrow 0$
then, R' , G' can be made small and negligible

If $R' \ll \omega L'$ and $G' \ll \omega C'$, then we can set
 $R' = G' \cong 0$

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$\gamma = \alpha + j\beta = j\omega\sqrt{L'C'} \longrightarrow \text{Lossless line}$$

$$\alpha = 0, \quad \beta = \omega\sqrt{L'C'}$$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \frac{R' + j\omega L'}{\sqrt{G' + j\omega C'}} = \sqrt{\frac{L'}{C'}} = Z_0$$

Lossless Transmission Line

For lossless transmission line:

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{L'C'}} \quad u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}$$

Recall: all TEM lines $L'C' = \mu\epsilon$

Then: $\beta = \omega\sqrt{\mu\epsilon} \frac{\text{rad}}{\text{m}}$ where μ, ϵ -- dielectric
usually $\mu = \mu_0$

$$u_p = \frac{1}{\sqrt{\mu\epsilon}} \text{ m/s}$$

$$\epsilon = \epsilon_r \epsilon_0$$

$$u_p = \frac{1}{\sqrt{\mu_0 \epsilon_r \epsilon_0}} = \frac{1}{\sqrt{\mu_0 \epsilon_0}} \frac{1}{\sqrt{\epsilon_r}} = \frac{c}{\sqrt{\epsilon_r}}$$

If $\epsilon_r = 1$, then $u_p = c$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}} = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

Lossless Transmission Line

$$\text{Define } \epsilon_r = \frac{\epsilon}{\epsilon_0}, \quad u_p = \frac{1}{\sqrt{\mu_0 \epsilon_r \epsilon_0}} = \frac{1}{\sqrt{\mu_0 \epsilon_0}} \cdot \frac{1}{\sqrt{\epsilon_r}} = \frac{c}{\sqrt{\epsilon_r}},$$

$$\text{Guided wavelength, } \lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}} = \frac{\lambda_0}{\sqrt{\epsilon_r}} \quad \text{In air (or vacuum) } \lambda_0 = \frac{c}{f}$$

If ϵ_r is independent of frequency \rightarrow non-dispersive

u_p is independent of frequency, no dispersion


Same phase velocity for all frequency components

\rightarrow Short pulse \rightarrow more frequencies,
dispersion is more critical at high data rates

TL– characteristic parameters -- Summary

	Propagation Constant $\gamma = \alpha + j\beta$	Phase Velocity u_p	Characteristic Impedance Z_0
General Case:	$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$ $\mu = \mu_0, \epsilon = \epsilon_r \epsilon_0, \quad c = \frac{1}{\sqrt{\mu_0 \epsilon_0}}, \quad \sqrt{\frac{\mu_0}{\epsilon_0}} \approx 120\pi \Omega$ (free space)	$u_p = \frac{\omega}{\beta}$	$Z_0 = \sqrt{\frac{(R' + j\omega L')}{(G' + j\omega C')}}}$
Lossless ($R' = G' = 0$)	$\gamma = j\beta \quad (\alpha = 0)$ $\beta = \frac{\omega \sqrt{\epsilon_r}}{c}$ Non-dispersive line: ϵ_r of insulator is independent of frequency	$u_p = \frac{c}{\sqrt{\epsilon_r}}$	$Z_0 = \sqrt{\frac{L'}{C'}}$
Lossless coax	$\alpha = 0$ $\beta = \frac{\omega \sqrt{\epsilon_r}}{c}$	$u_p = \frac{c}{\sqrt{\epsilon_r}}$	$Z_0 = \frac{60}{\sqrt{\epsilon_{eff}}} \ln\left(\frac{b}{a}\right)$ $z_0 = \sqrt{\frac{\frac{\mu}{2\pi} \ln(\frac{b}{a})}{\frac{2\pi\epsilon}{\ln(\frac{b}{a})}}} = \sqrt{\frac{\mu}{\epsilon}} \frac{1}{2\pi} \ln\left(\frac{b}{a}\right)$

TL– characteristic parameters -- Summary

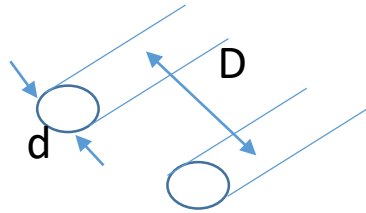	Propagation Constant $\gamma = \alpha + j\beta$	Phase Velocity u_p	Characteristic Impedance Z_0
Lossless 2-wire:	$\alpha = 0 \quad \beta = \frac{\omega\sqrt{\epsilon_r}}{c}$	$u_p = \frac{c}{\sqrt{\epsilon_r}}$	$Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln\left[\left(\frac{D}{d}\right) + \sqrt{\left(\frac{D}{d}\right)^2 - 1}\right]$
			
Lossless parallel-plate	$\alpha = 0 \quad \beta = \frac{\omega\sqrt{\epsilon_r}}{c}$	$u_p = \frac{c}{\sqrt{\epsilon_r}}$	$Z_0 = \frac{120\pi}{\sqrt{\epsilon_r}} \left(\frac{h}{w}\right)$ <div> <div>separation</div> <div>Plate width</div> </div>