

ELEN E3401: Electromagnetics

Spring 2025

Prof. Keren Bergman

Lecture #6



COLUMBIA | ENGINEERING
The Fu Foundation School of Engineering and Applied Science



Lossless Transmission Line

Consider lossless line, $\gamma = j\beta$

Examine these wave solutions of wave equations:


$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0$$

$$\frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0$$

$$\tilde{V}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$
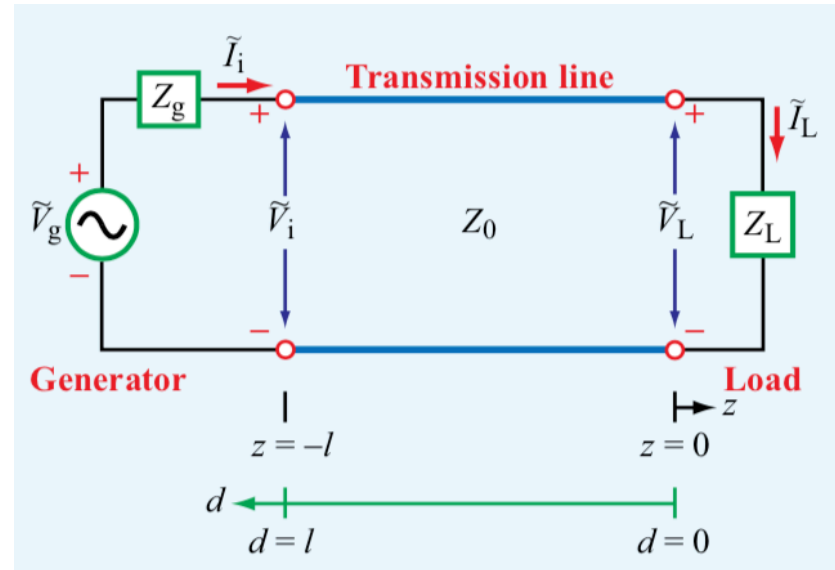
$$\Gamma = \frac{V_0^-}{V_0^+} \longrightarrow V_0^- = \Gamma V_0^+$$



$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$$

Solutions have $+z$ and $-z$ wave components

Standing Waves

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

Compute $|\tilde{V}(z)| \rightarrow$ the magnitude of $\tilde{V}(z)$


$$|\tilde{V}(z)| = |\tilde{V}(z)\tilde{V}(z)^*|^{1/2}$$

$$|\tilde{V}(z)| = \{ [V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z})] \times [(V_0^+)^* (e^{j\beta z} + |\Gamma| e^{-j\theta_r} e^{-j\beta z})] \}^{1/2}$$

$$= |V_0^+| [1 + |\Gamma|^2 + |\Gamma| (e^{j(2\beta z + \theta_r)} + e^{-j(2\beta z + \theta_r)})]^{1/2} \longleftarrow e^{jx} + e^{-jx} = 2\cos(x)$$

$$= |V_0^+| [1 + |\Gamma|^2 + 2|\Gamma|\cos(2\beta z + \theta_r)]^{1/2}$$

Standing Waves

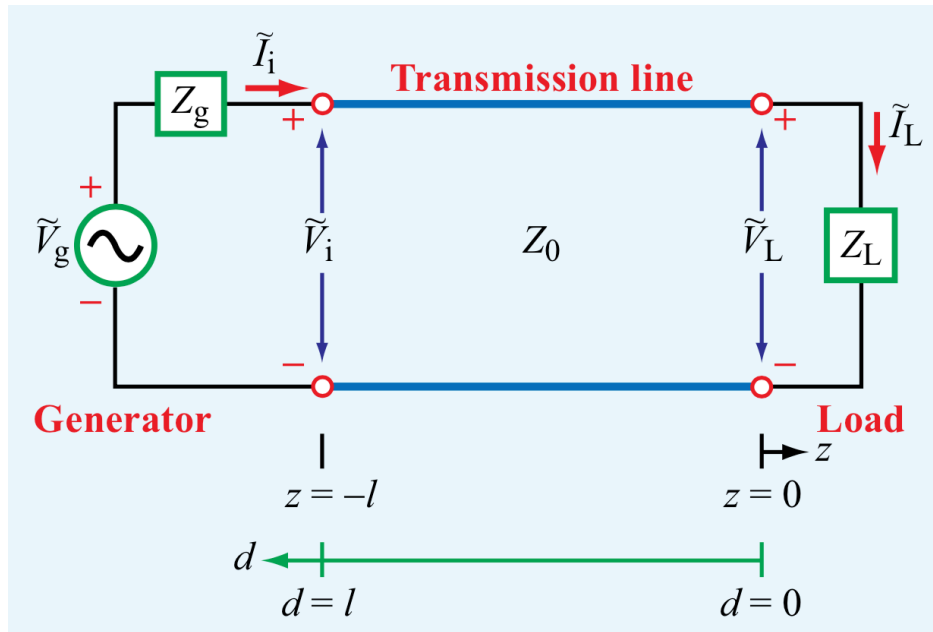

Load at $z = 0$

Generator at $z = -l$
 $d = -z$

Express \tilde{V} as function of (d) instead of (z) $z \rightarrow -d$

$$|\tilde{V}(d)| = |V_0^+| [1 + |\Gamma|^2 + 2|\Gamma|\cos(2\beta d - \theta_r)]^{1/2}$$

We also obtain similar equations for $|\tilde{I}(d)|$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} [1 + |\Gamma|^2 - 2|\Gamma|\cos(2\beta d - \theta_r)]^{1/2}$$

Standing Waves

$|\tilde{V}(d)|$ and $|\tilde{I}(d)|$ are standing waves

→ result of interference of two travelling waves components

Maximum value of standing wave occurs when incident and reflection components are in-phase:

$$|\tilde{V}(d)| = |V_0^+| [1 + |\Gamma|^2 + 2|\Gamma|\cos(2\beta d - \theta_r)]^{1/2}$$

$$|\tilde{V}(d)| \text{ max occurs when: } (2\beta d - \theta_r = 2n\pi)$$

Consider example: $|V_0^+| = 1V$, $Z_0 = 50 \Omega$, $\Gamma = 0.3e^{j30^\circ}$

$$|\Gamma| = 0.3, \theta_r = 30^\circ$$

$$|\tilde{V}|_{\max} = (1 + |\Gamma|)|V_0^+| = 1.3V$$

Standing Waves

Minimum value of $|\tilde{V}(d)|$ occurs when two waves, incident and reflective interfere destructively – opposite phase:

$$|\tilde{V}|_{\min} \text{ occurs when: } (2\beta d - \theta_r = (2n + 1)\pi)$$

$$|\tilde{V}|_{\min} = (1 - |\Gamma|)|V_0^+| = 0.7V$$


Note: spatial (λ) of standing wave = $\lambda/2$

$|\tilde{V}(d)|$ and $|\tilde{I}(d)|$ are opposite phase:

$$|\tilde{V}(d)| = |V_0^+| [1 + |\Gamma|^2 + 2|\Gamma|\cos(2\beta d - \theta_r)]^{1/2}$$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} [1 + |\Gamma|^2 - 2|\Gamma|\cos(2\beta d - \theta_r)]^{1/2}$$

Standing Waves

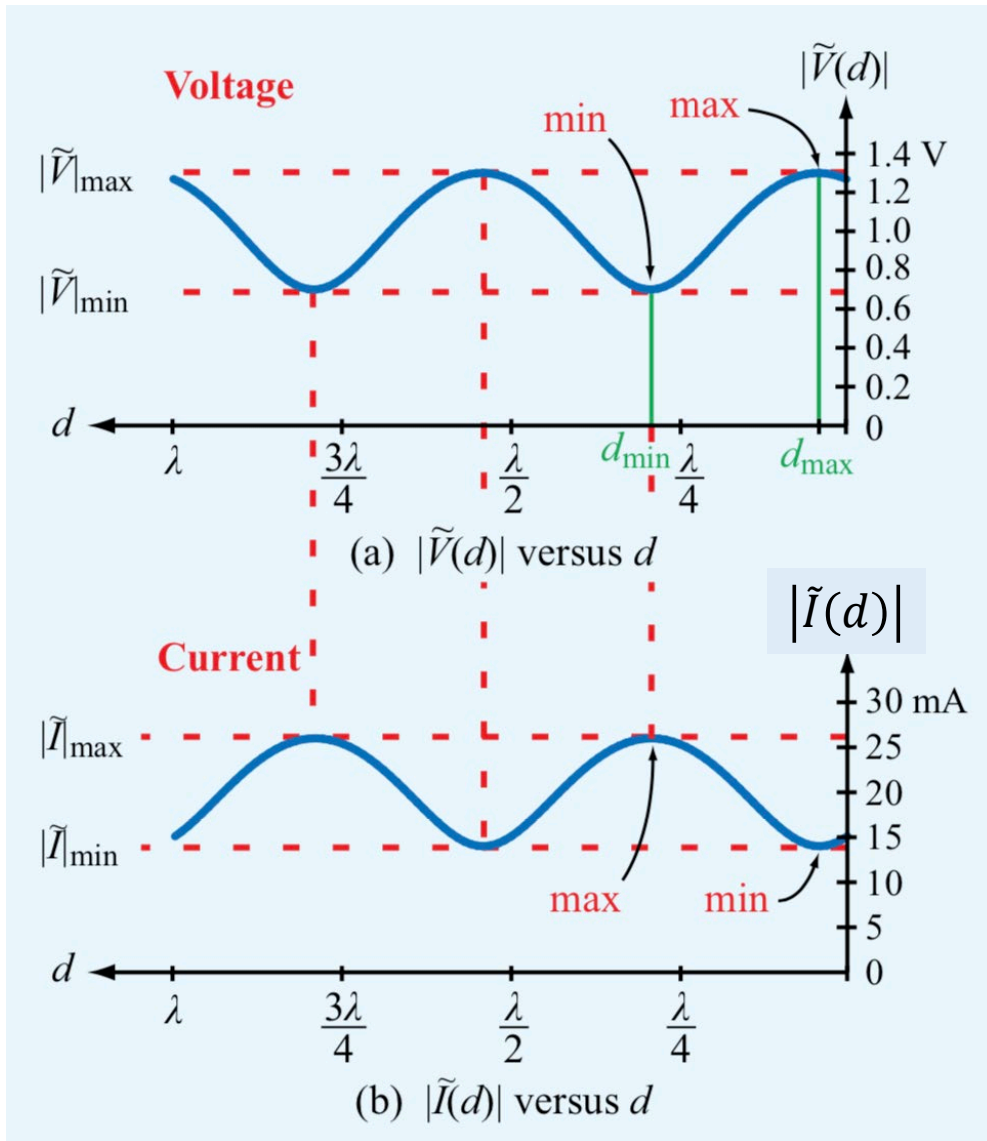

Example of $|\tilde{V}(d)|$ and $|\tilde{I}(d)|$ shown for transmission line with:

$$|V_0^+| = 1V, \quad |\Gamma| = 0.3, \\ Z_0 = 50\ \Omega, \quad \theta_r = 30^\circ$$

$$Z_0 = 50\ \Omega \quad \Gamma = 0.3e^{j30^\circ}$$

$$|\tilde{V}|_{max} = (1 + |\Gamma|)|V_0^+| = 1.3V$$

$$|\tilde{V}|_{min} = (1 - |\Gamma|)|V_0^+| = 0.7V$$

$$S = \frac{|\tilde{V}_{max}|}{|\tilde{V}_{min}|} = \frac{1.3}{0.7}$$

Voltage Standing Waves

Standing wave with maxima $2 |V_0^+|$

$$|\tilde{V}(d)| = |V_0^+| [1 + |\Gamma|]$$

$$2\beta d_{max} - \theta_r = 2\pi n$$

$$d_{max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2} \quad \beta = \frac{2\pi}{\lambda}$$
$$\left\{ \begin{array}{l} n = 1, 2, \dots \text{ if } \theta_r < 0, \\ n = 0, 1, 2, \dots \text{ if } \theta_r \geq 0. \end{array} \right. \quad -\pi \leq \theta_r \leq \pi$$

If $\theta_r \geq 0$ - then first voltage maximum, at $n = 0$ occurs at:

$$d_{max} = \frac{\theta_r \lambda}{4\pi}$$

If $\theta_r < 0$ - then first voltage maximum, at $n = 1$ occurs at:

$$d_{max} = \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}$$

Voltage Standing Waves

$|\tilde{V}|_{min} \rightarrow$ will occur when \cos argument $= (2n+1)\pi$

$$|\tilde{V}|_{min} = |V_0^+|(1 - |\Gamma|)$$

when $2\beta d_{min} - \theta_r = (2n + 1)\pi$

$-\pi \leq \theta_r \leq \pi \rightarrow$ then first minimum occurs at $n = 0$, or $\frac{\lambda}{4}$ from d_{max}

$$d_{min} = \begin{cases} d_{max} + \frac{\lambda}{4}, & \text{if } d_{max} < \frac{\lambda}{4} \\ d_{max} - \frac{\lambda}{4}, & \text{if } d_{max} \geq \frac{\lambda}{4} \end{cases}$$

Voltage Standing Wave Ratio

(Dimensionless)

$$S = \frac{|\tilde{V}|_{max}}{|\tilde{V}|_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

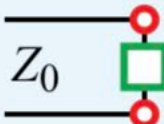
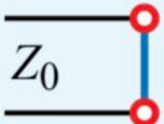
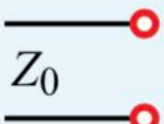

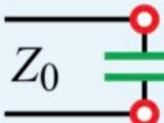
VSWR or SWR

This is a measure of load mismatch versus matched load.


Matched load: $\Gamma = 0 \rightarrow S = 1$

For $|\Gamma|=1 \rightarrow S = \infty$


Reflection Coefficient: $\Gamma = |\Gamma|e^{j\theta_r}$

Load	$ \Gamma $	θ_r
 Z_0 (Matched Load)	0 (no reflection)	irrelevant
 Z_0 (short)	1	$\pm 180^\circ$ (phase opposition)
 Z_0 (open)	1	0 (in-phase)
 $jX = j\omega L$ (Inductive Load)	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $jX = \frac{-j}{\omega C}$ (Capacitive Load)	1	$\pm 180^\circ + 2 \tan^{-1} x$


Voltage Standing Waves

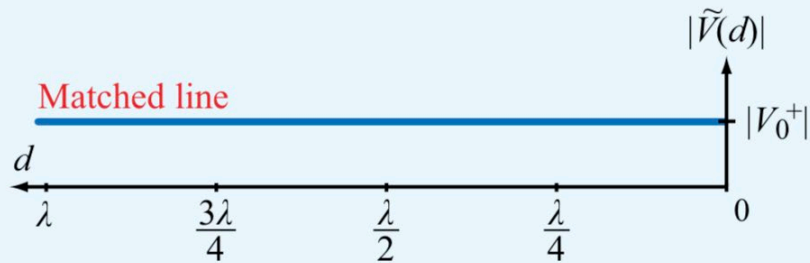

(a) $Z_L = Z_0$

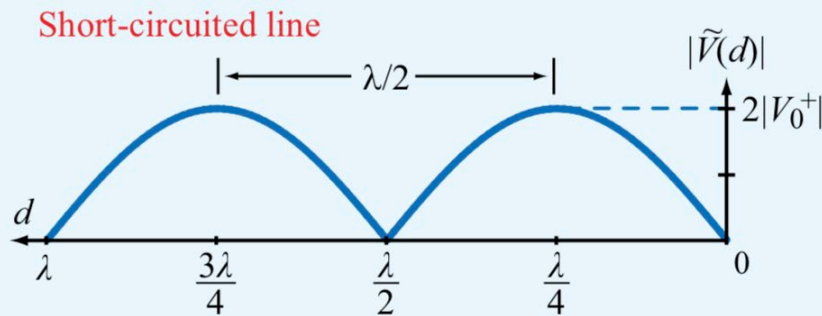

(b) $Z_L = 0$ (short circuit)

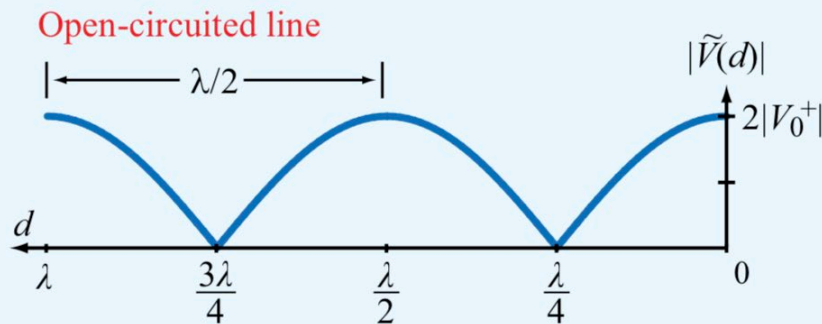

(c) $Z_L = \infty$ (open circuit)

1. Matched line $Z_L = Z_0$, $|\Gamma|=0$


$$|\tilde{V}(d)| = |V_0^+| \quad \text{for all } d$$

2. Short circuit $Z_L = 0$, $|\Gamma|=1$, $\Gamma = -1$

3. Open circuit $Z_L = \infty$, $|\Gamma|=1$, $\Gamma = 1$


Reflection Coefficient $\Gamma = |\Gamma|e^{j\theta_r}$

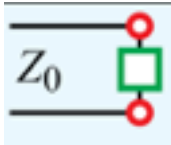Load - general $z_L = \frac{Z_L}{Z_0} = \frac{R + jX}{Z_0} = r + jx$



$$Z_L = (r + jx)Z_0 \quad |\Gamma| = \left[\frac{(r - 1)^2 + x^2}{(r + 1)^2 + x^2} \right]^{1/2}$$

$$r = \frac{R}{Z_0}$$

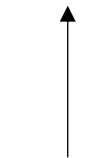

Real

$$x = \frac{X}{Z_0}$$



Imaginary

of z_L

$$\theta_r = \tan^{-1} \left(\frac{x}{r - 1} \right) - \tan^{-1} \left(\frac{x}{r + 1} \right)$$

Example: purely reactive load

Q: Show $|\Gamma| = 1$ for lossless line connected to a purely reactive load

$$Z_L = jX_L \quad \Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX_L - Z_0}{jX_L + Z_0}$$

$$\Gamma = \frac{-(Z_0 - jX_L)}{Z_0 + jX_L} = \frac{-\sqrt{Z_0^2 + X_L^2} e^{-j\theta}}{\sqrt{Z_0^2 + X_L^2} e^{j\theta}} \quad \text{Note: } \theta = \tan^{-1}\left(\frac{X_L}{Z_0}\right)$$

$$\Gamma = -e^{-j2\theta}$$
$$|\Gamma| = \sqrt{e^{-j2\theta} e^{j2\theta}} \quad \text{Note: } |z| = \sqrt{zz^*}$$

$$|\Gamma| = 1$$