

ELEN E3401: Electromagnetics

Spring 2025

Prof. Keren Bergman

Lecture #7



COLUMBIA | ENGINEERING
The Fu Foundation School of Engineering and Applied Science




Wave Impedance – Lossless Line

When impedance not matched →
we have standing waves and voltage is out of phase with current.

We define the wave impedance:
ratio of the total voltage to the total current at any point, d , on the line.

Wave impedance:
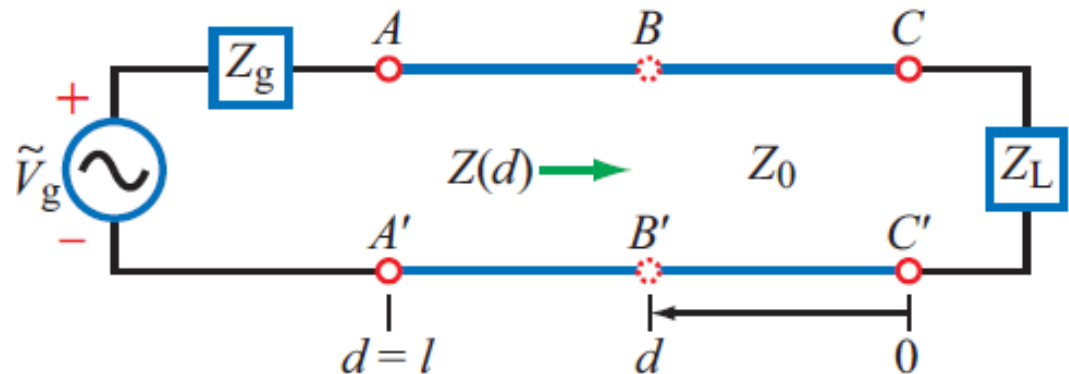
$$Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)}$$



Note: this is **not** Z_0 which is the voltage/current ratio of individual wave amplitudes.

$$Z_0 = \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-}$$

Wave Impedance – Lossless Line

Wave impedance: $Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)}$


Recall: $\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$ (wave equation solution)

Lossless $\rightarrow \tilde{V}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$


Then $z = -d$,
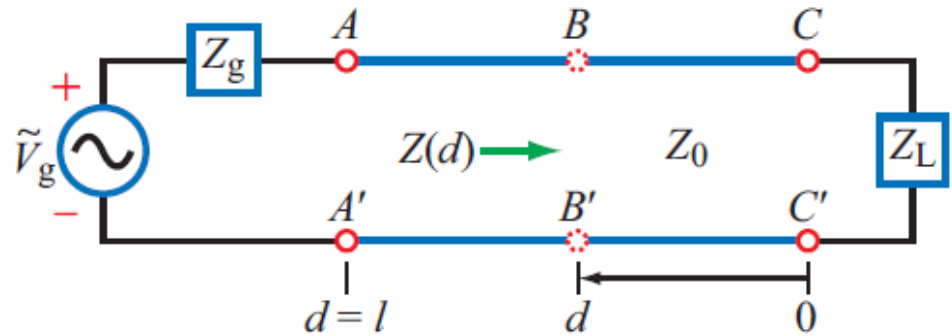
$$Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+ (e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0$$



Wave Impedance – Lossless Line

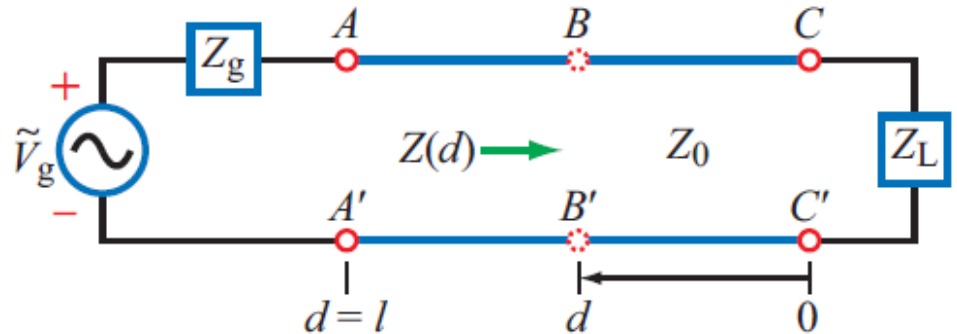Wave impedance: $Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)}$



$$Z(d) = Z_0 \left(\frac{e^{j\beta d} + \Gamma e^{-j\beta d}}{e^{j\beta d} - \Gamma e^{-j\beta d}} \right) \times \frac{e^{-j\beta d}}{e^{-j\beta d}}$$


$$Z(d) = Z_0 \left(\frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right) = Z_0 \left(\frac{1 + \Gamma_d}{1 - \Gamma_d} \right)$$

Define: $\Gamma_d = e^{-j2\beta d} \Gamma = |\Gamma| e^{j(\theta_r - 2\beta d)} \rightarrow$ voltage reflection ratio, Γ , phase shifted by $2\beta d$

$$(\Gamma_d = e^{-j2\beta d} \Gamma = |\Gamma| e^{j\theta_r - j2\beta d})$$

Wave Impedance – Lossless Line

Consider the transmission line circuit:

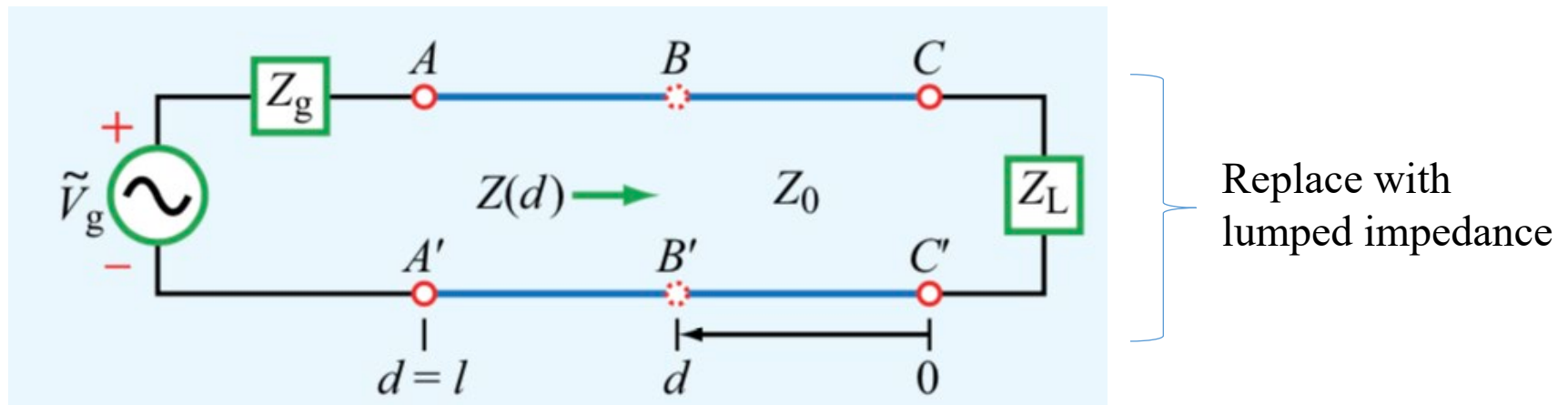


Terminals BB' are at arbitrary location d on the line, $Z(d)$:

wave impedance of line when “looking” toward load


Wave Impedance – Lossless Line

Consider the transmission line circuit:

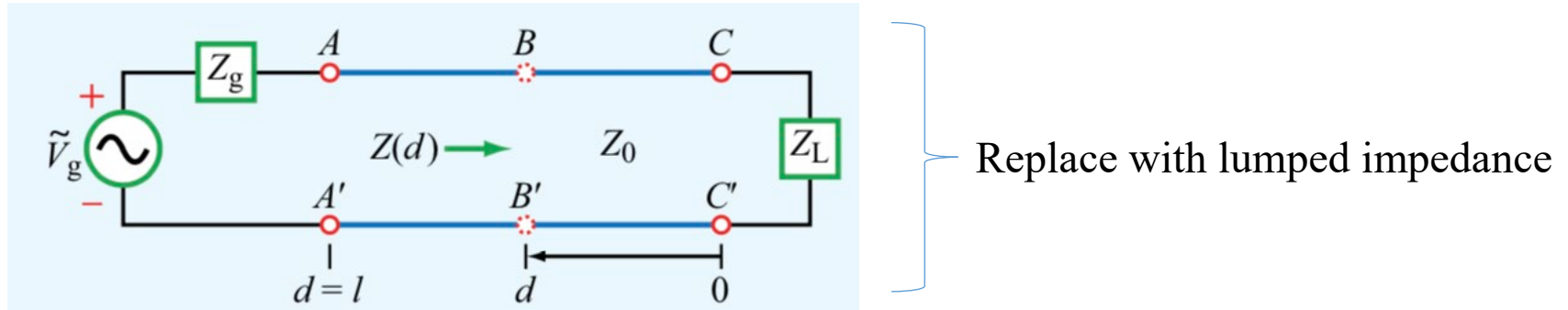


We use equivalent circuit:

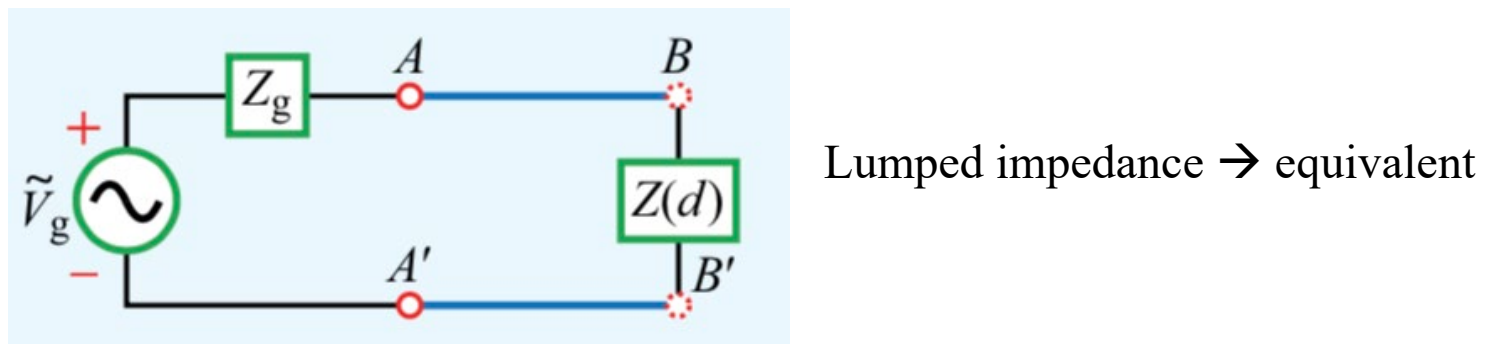Replace segment to right of BB' with lumped impedance $\rightarrow Z(d)$



Wave Impedance – Lossless Line

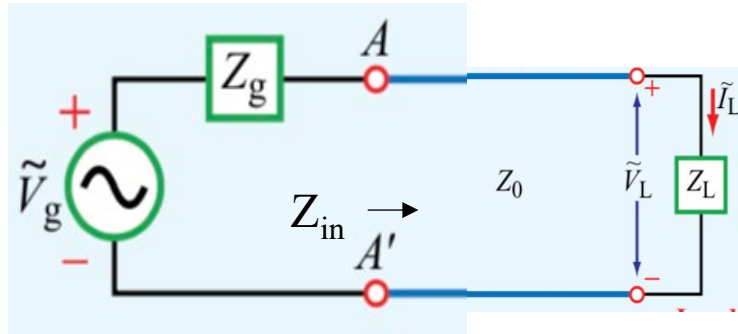

An important value is the input impedance at the source end of line, at $d = l$

$$Z_{in} = Z(l) = Z_0 \left(\frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

Define: $\Gamma_l = e^{-j2\beta l} \Gamma = |\Gamma| e^{j\theta_r - j2\beta l}$

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


Using relations: $e^{j\beta l} = \cos(\beta l) + j\sin(\beta l)$

$$e^{-j\beta l} = \cos(\beta l) - j\sin(\beta l)$$

We obtain:

$$Z_{in} = Z_0 \left(\frac{z_L \cos(\beta l) + j\sin(\beta l)}{\cos(\beta l) + jz_L \sin(\beta l)} \right) = Z_0 \left(\frac{z_L + j\tan(\beta l)}{1 + jz_L \tan(\beta l)} \right)$$


Wave Impedance – Lossless Line

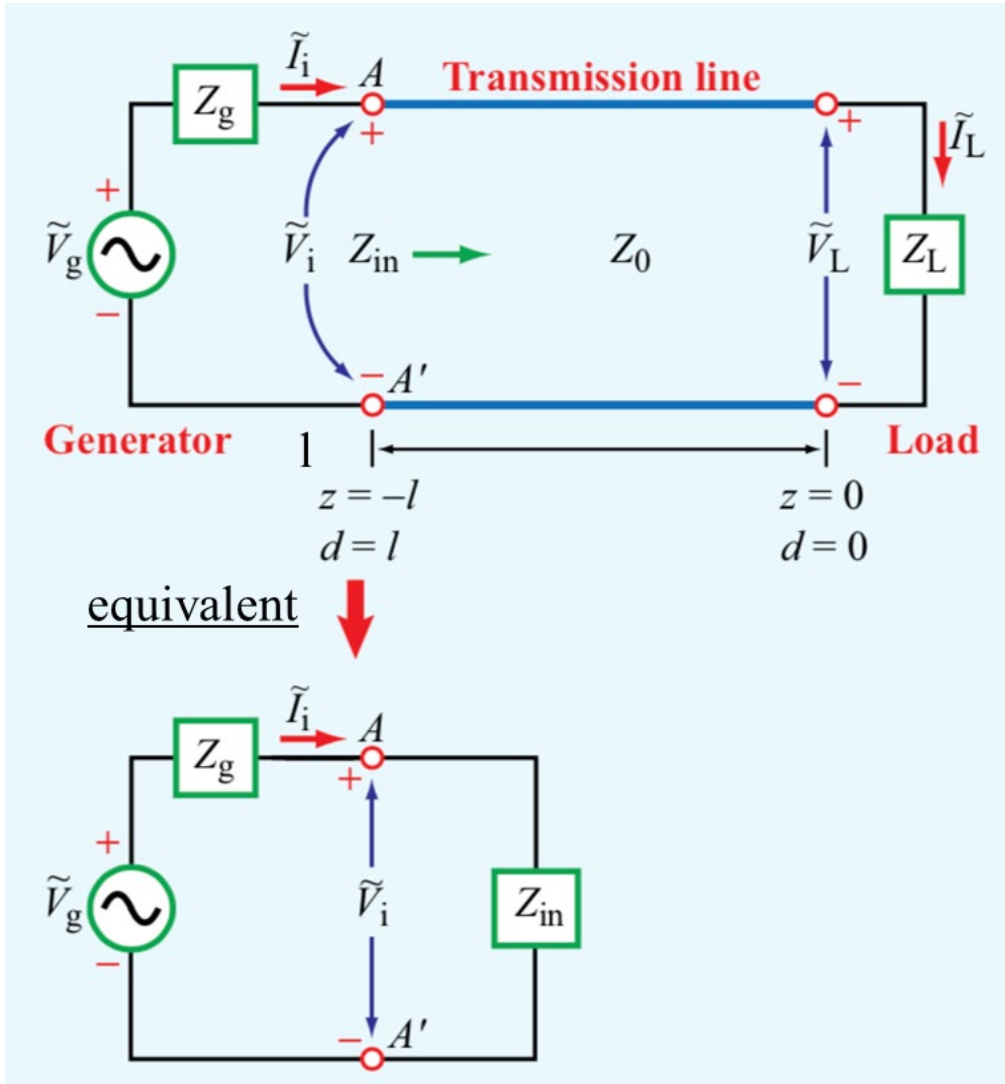

At generator (source) end:

replace transmission line + load
with input impedance = Z_{in}

Wave Impedance – Lossless Line

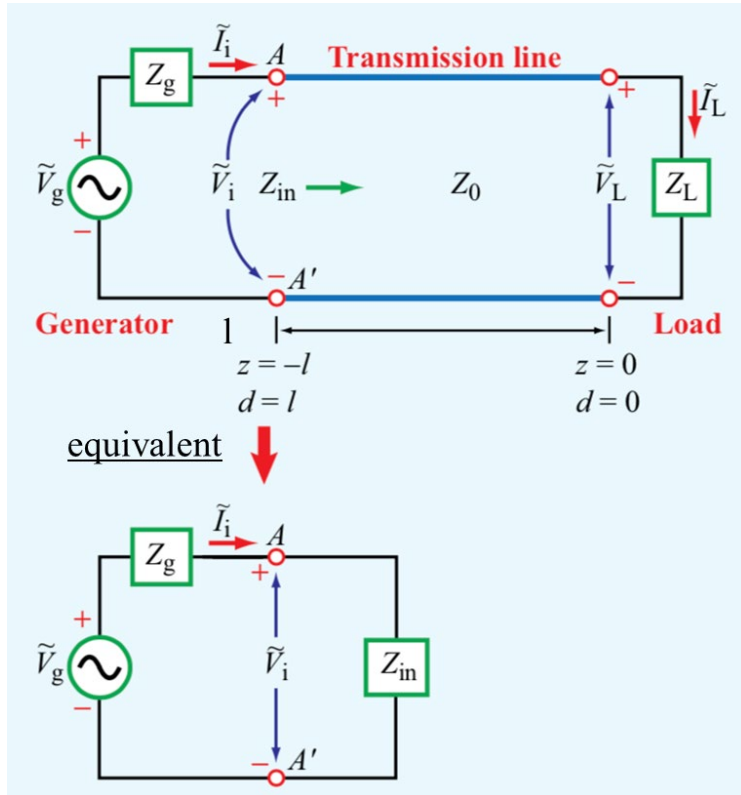

From generator: (transmission line replaced with impedance Z_{in})

$$\tilde{V}_i = \tilde{I}_i Z_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}}$$

From transmission line:
(at input to line) \rightarrow voltage:

$$\tilde{V}_i = \tilde{V}_i$$

Phasor voltage across Z_{in} equivalent at interface

$$\tilde{V}_i = \tilde{V}(-l) = V_0^+ (e^{j\beta l} + \Gamma e^{-j\beta l}) \quad (\text{at } z = -l)$$

Solve for V_0^+ :

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right)$$

$$Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+ (e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0$$

Transmission Line Recap

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0 \quad \frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0$$

Wave solution equations = traveling wave

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

4 unknowns: $V_0^+, V_0^-, I_0^+, I_0^-$

$$Z_0 = \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-}$$

Reduced to 2 unknowns
by transmission line
lumped element model

Transmission Line Recap

Applying boundary condition at load, we can relate V_0^- to V_0^+ through Γ

Applying boundary condition at source, \rightarrow obtain expression for V_0^+

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right)$$

$$\text{From Load: } Z(d) = Z_0 \left(\frac{1 + \Gamma_d}{1 - \Gamma_d} \right) \quad Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+ (e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0$$

$$\text{where } \Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r - j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$$

$$\text{From Source: } Z(l) = Z_0 \left(\frac{1 + \Gamma_l}{1 - \Gamma_l} \right) \quad \Gamma_l = \Gamma e^{-j2\beta l} = |\Gamma| e^{j(\theta_r - 2\beta l)}$$

$$Z_{in} = Z(l = d) = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$

$$\tilde{V}_i = \tilde{I}_i Z_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = V_0^+ (e^{j\beta l} + \Gamma e^{-j\beta l})$$

Example – solutions for $v(d,t)$ and $i(d,t)$


Example:

Generator ($f = 1.05\text{GHz}$) circuit with $v_g(t) = 10\sin(\omega t + 30^\circ)$

Connected to load: $Z_L = (100 + j50)\ \Omega$

through lossless transmission line of length $l = 67\text{ cm}$ and $Z_0 = 50\ \Omega$

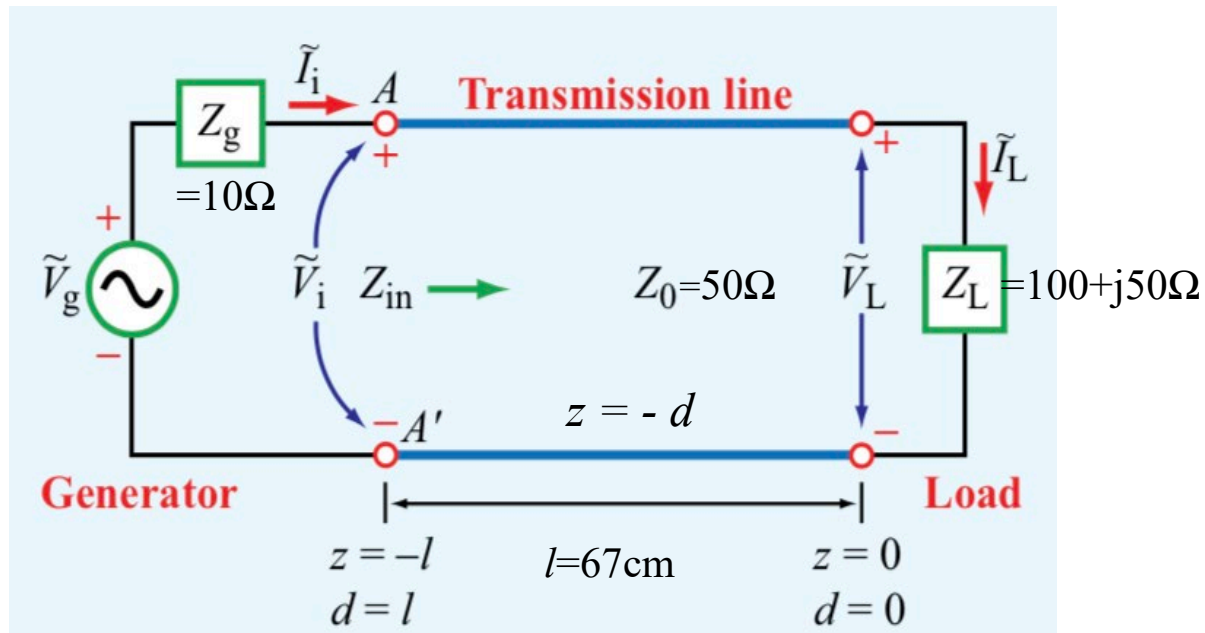
$Z_g = 10\ \Omega$ and the phase velocity of line $u_p = 0.7c$



Find: $v(d,t)$ and $i(d,t)$

Example – solutions for $v(d,t)$ and $i(d,t)$


Find: $v(d,t)$ and $i(d,t)$

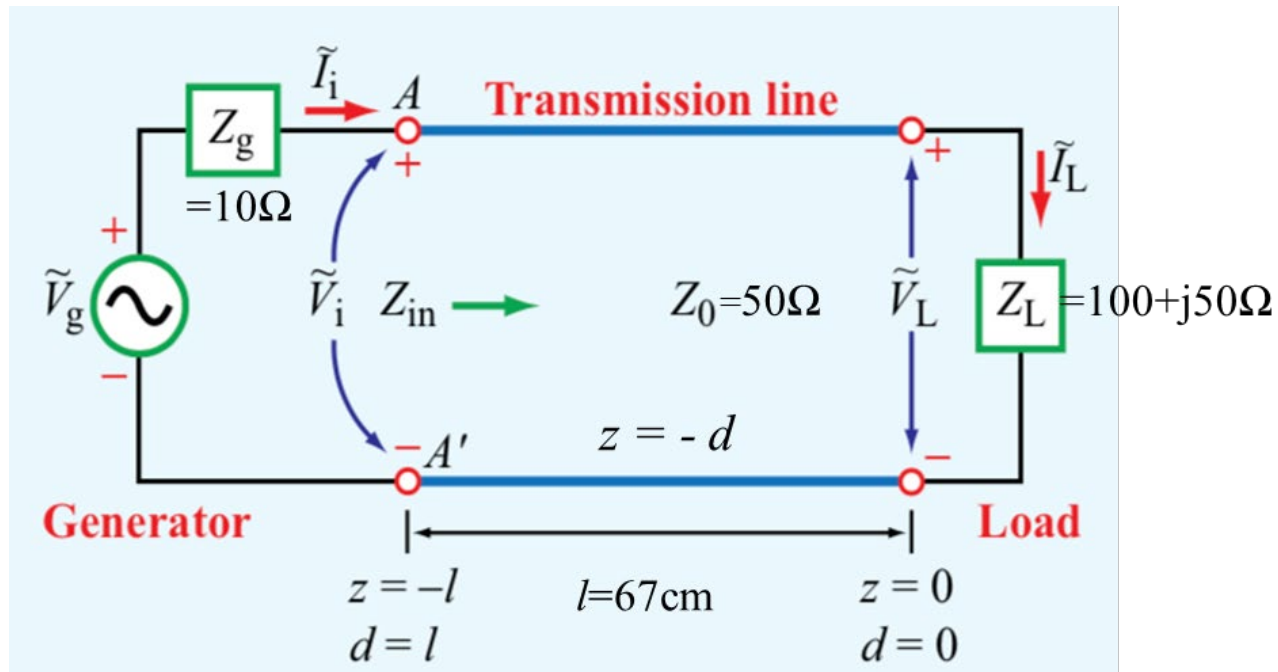

Strategy: we will find $\tilde{V}(d) \rightarrow$ then get time domain, $v(d,t)$

Example – solutions for $v(d,t)$ and $i(d,t)$

Find: $v(d,t)$ and $i(d,t)$

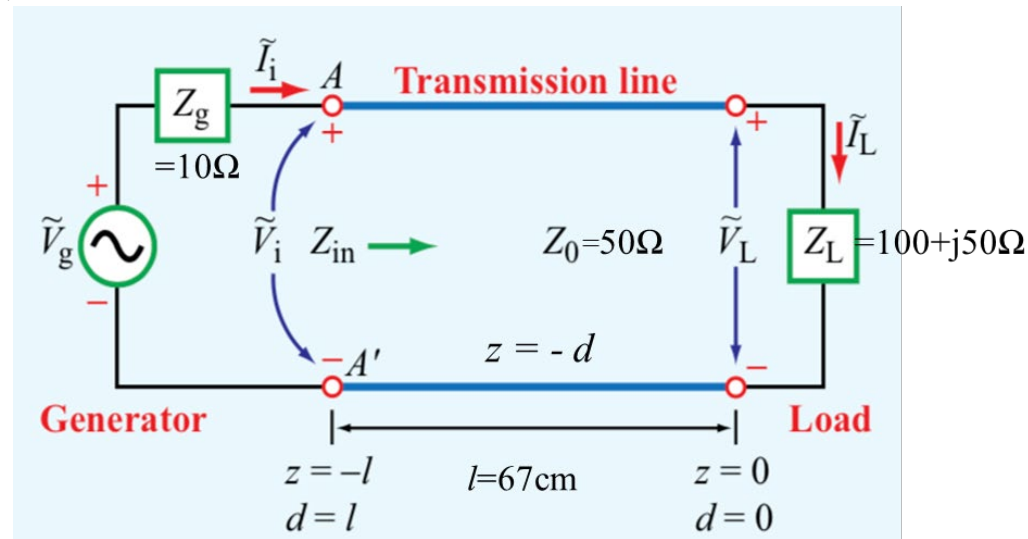

Is our TL lossless?

$$\text{To get } \tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})$$


Lossless line solution

Need to find V_0^+ :

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right) \quad \text{Need to obtain, } \tilde{V}_g, Z_{in}, \Gamma, \beta$$

Example – solutions for $v(d,t)$ and $i(d,t)$

Starting with getting β : $\beta = \frac{2\pi}{\lambda}$ $u_p = \lambda f$


$$\lambda = \frac{u_p}{f} = \frac{0.7 \times 3 \times 10^8}{1.05 \times 10^9} = 0.2m$$

$$\beta = \frac{2\pi}{0.2} = 10\pi$$

$$\beta l = \frac{2\pi}{\lambda} l = \frac{2\pi}{0.2} (0.67) = 6.7\pi$$

$$\beta l = 6.7\pi - 6\pi = 0.7\pi \rightarrow 126^\circ$$

Example – solutions for $v(d,t)$ and $i(d,t)$

Now obtain, Γ

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 + j50) - 50}{(100 + j50) + 50} = 0.45e^{j26.6^\circ}$$

$$Z_{in} = Z(l)$$

$$= Z_0 \left(\frac{1 + \Gamma_l}{1 - \Gamma_l} \right) = Z_0 \left(\frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right) \quad \Gamma_l = \Gamma e^{-j2\beta l}$$

$$= 50 \left(\frac{1 + 0.45e^{j26.6^\circ} e^{-j252^\circ}}{1 - 0.45e^{j26.6^\circ} e^{-j252^\circ}} \right)$$

$$Z_{in} = (21.9 + j17.4) \, \Omega$$

Example – solutions for $v(d,t)$ and $i(d,t)$

Now obtain, \widetilde{V}_g $v_g(t) = 10\sin(\omega t + 30^\circ)$

$$v_g(t) = \operatorname{Re}[\widetilde{V}_g e^{j\omega t}]$$

Need to move to
cosine reference

$$v_g(t) = 10 \cos(90^\circ - \omega t - 30^\circ) = 10 \cos(\omega t - 60^\circ)$$

$$v_g(t) = \operatorname{Re} \left[10e^{-j60^\circ} e^{j\omega t} \right] \quad \widetilde{V}_g = 10 \angle -60^\circ$$

Example – solutions for $v(d,t)$ and $i(d,t)$

Now, obtain V_0^+ :

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right)$$

$$V_0^+ = \left(\frac{10e^{-j60^\circ} (21.9 + j17.4)}{10 + (21.9 + j17.4)} \right) \left(\frac{1}{e^{j126^\circ} + 0.45e^{j26.6^\circ} e^{-j126^\circ}} \right)$$

$$V_0^+ = 10.2e^{j159^\circ} \text{ (V)}$$

$$\tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})$$

$$\tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d}) = 10.2e^{j159^\circ} (e^{j\beta d} + 0.45e^{j26.6^\circ} e^{-j\beta d})$$

Example – solutions for $v(d,t)$ and $i(d,t)$

Now convert to time domain:

$$v(d,t) = \text{Re}[\tilde{V}(d)e^{j\omega t}]$$

$$v(d,t) = 10.2\cos(\omega t + \beta d + 159^\circ) + 4.55\cos(\omega t - \beta d + 185.6^\circ)$$

We can then obtain $\tilde{I}(d)$ and $i(d,t)$:

$$\tilde{I}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} - \Gamma e^{-j\beta d})$$

$$\tilde{I}(d) = 0.20e^{j159^\circ} (e^{j\beta d} - 0.45e^{j26.6^\circ} e^{-j\beta d})$$

$$i(d,t) = 0.20\cos(\omega t + \beta d + 159^\circ) - 0.09\cos(\omega t - \beta d + 185.6^\circ)$$