

# ELEN E3401: Electromagnetics

Spring 2025

Prof. Keren Bergman

Lecture #8



**COLUMBIA | ENGINEERING**  
The Fu Foundation School of Engineering and Applied Science



# Wave Impedance - summary

Wave impedance:  $Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = Z_0 \left( \frac{1+\Gamma_d}{1-\Gamma_d} \right) \quad \Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$


Input impedance at  $d = l$  :

$$Z_{in} = Z(l) = Z_0 \left( \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right) = Z_0 \left( \frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right) \quad z_L = \frac{Z_L}{Z_0}$$

We obtain solution:

$$V_0^+ = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right)$$

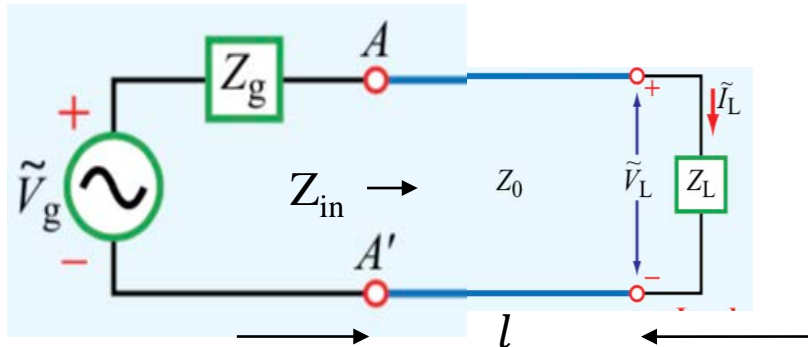Now we can obtain full  $v(d,t)$ ,  $i(d,t)$  Solutions: given  $V_g(t) \rightarrow \tilde{V}_g$ ,  $Z_g, Z_0, Z_L$ , length TL



obtain  $\rightarrow \tilde{V}_g, Z_{in}, \Gamma, \beta$

# Special cases of lossless TL

---

$$\tilde{V}(d) = V_0^+(e^{j\beta d} + \Gamma e^{-j\beta d}) \quad \tilde{I}(d) = \frac{V_0^+}{Z_0} V_0^+(e^{j\beta d} - \Gamma e^{-j\beta d})$$

$$Z(d) = Z_0 \left( \frac{1 + \Gamma_d}{1 - \Gamma_d} \right) \quad Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+(e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+(e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0$$

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r - j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$$

## Special cases of lossless TL: short circuit

---

$$\tilde{V}(d) = V_0^+(e^{j\beta d} + \Gamma e^{-j\beta d}) \quad \tilde{I}(d) = \frac{V_0^+}{Z_0} V_0^+(e^{j\beta d} - \Gamma e^{-j\beta d})$$

$$Z(d) = Z_0 \left( \frac{1 + \Gamma_d}{1 - \Gamma_d} \right) \quad Z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+(e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+(e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0$$

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r - j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Short Circuit:  $Z_L = 0, \Gamma = -1$ :

$$\tilde{V}_{sc}(d) = V_0^+(e^{j\beta d} - e^{-j\beta d}) = 2jV_0^+ \sin(\beta d)$$

$$\tilde{I}_{sc}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} + e^{-j\beta d}) = \frac{2V_0^+}{Z_0} \cos(\beta d)$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)} = jZ_0 \tan(\beta d)$$

## Special cases of lossless TL: short circuit

---

$$\tilde{V}_{sc}(d) = V_0^+(e^{j\beta d} - e^{-j\beta d}) = 2jV_0^+ \sin(\beta d)$$

$$\tilde{I}_{sc}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} + e^{-j\beta d}) = \frac{2V_0^+}{Z_0} \cos(\beta d)$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)} = jZ_0 \tan(\beta d)$$

→ The voltage  $\tilde{V}_{sc}(d) = 0$  at  $d = 0$  (load) → short circuit

Then as we go away from load the voltage amplitude will vary as:  $\sin(\beta d)$


**Note**: this is the amplitude, not  $|\tilde{V}(d)|$  which is a standing wave of  $\lambda/2$

→ The current amplitude  $\tilde{I}_{sc}(d)$  is maximum at load and varies as  $\cos(\beta d)$

→  $Z_{in}^{SC}$ : input impedance of short-circuited line of length  $l$ :

$$Z_{in}^{SC} = \frac{\tilde{V}_{sc}(l)}{\tilde{I}_{sc}(l)} = jZ_0 \tan(\beta l)$$
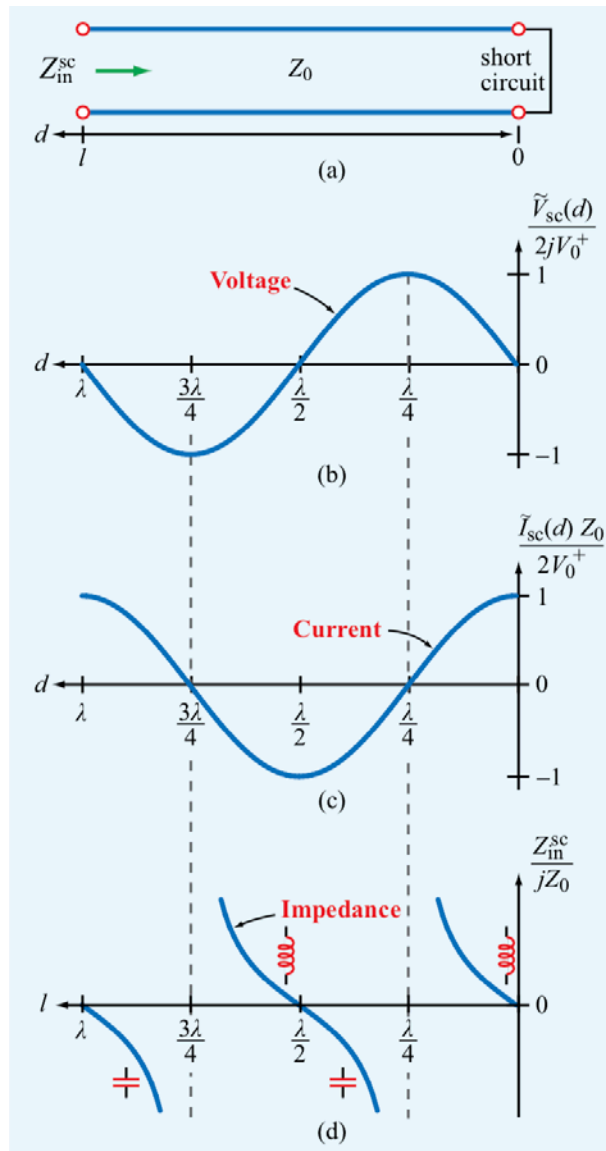
# Special cases of lossless TL: short circuit



$$Z_L = 0, \Gamma = -1, S = \infty$$

Normalized voltage amplitude


Normalized current amplitude

Normalized input impedance

# Special cases of lossless TL: short circuit

---

$$Z_{in}^{sc} = \frac{\tilde{V}_{sc}(l)}{\tilde{I}_{sc}(l)} = jZ_0 \tan(\beta l)$$

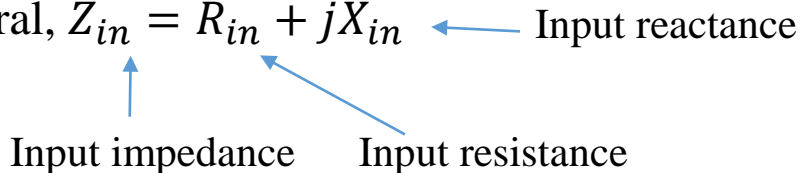In general,  $Z_{in} = R_{in} + jX_{in}$  

For short circuit,  $Z_{in} = jX_{in}$  (purely reactive)

For SC line, if  $l < \lambda/4$ , its impedance is equivalent to an inductor

If  $\lambda/4 < l < \lambda/2 \rightarrow$  impedance looks like a capacitor

$$Z_{in}^{sc} = jZ_0 \tan(\beta l) = jZ_0 \tan\left(\frac{2\pi \lambda}{\lambda} \frac{l}{8}\right) = jZ_0 \tan\left(\frac{\pi}{4}\right)$$

$$l < \frac{\lambda}{4}, \tan(\beta l) > 0 \quad Z_{in}^{sc} = jZ_0(\tan) \rightarrow \text{inductor}$$

$$\frac{\lambda}{4} \leq l < \frac{\lambda}{2}, \tan(\beta l) < 0 \quad Z_{in}^{sc} = -jZ_0(\tan) \rightarrow \text{capacitor}$$

# Special cases of lossless TL: short circuit

---

For  $\tan(\beta l) \geq 0 \rightarrow$  line appears inductive with equivalent inductance  $= L_{eq}$ ,

$$\begin{aligned} j\omega L_{eq} &= jZ_0 \tan(\beta l) \\ L_{eq} &= \frac{Z_0 \tan(\beta l)}{\omega} \quad (H) \end{aligned} \quad \text{if } \tan(\beta l) \geq 0$$

Minimum length of  $Z_{in}^{SC}$  equivalent to inductor:  $l = \frac{1}{\beta} \tan^{-1}\left(\frac{\omega L_{eq}}{Z_0}\right)$  (m)

For  $\tan(\beta l) \leq 0 \rightarrow$  input impedance is capacitive, line acts like equivalent capacitor,


$$\begin{aligned} \frac{1}{j\omega C_{eq}} &= jZ_0 \tan(\beta l) \\ C_{eq} &= \frac{1}{Z_0 \omega \tan(\beta l)} \quad (F) \end{aligned} \quad \text{if } \tan(\beta l) \leq 0$$

Shortest length of  $l$  for  $\tan(\beta l) \leq 0$  is:  $l = \frac{1}{\beta} \left[ \pi - \tan^{-1}\left(\frac{1}{\omega C_{eq} Z_0}\right) \right]$  (m)  $\frac{\pi}{2} \leq \beta l \leq \pi$

Make equivalent inductors and capacitors by designing length of short-circuited line

Common in high speed microwave circuits, fabricating inductors/capacitors more challenging than microstrip transmission line
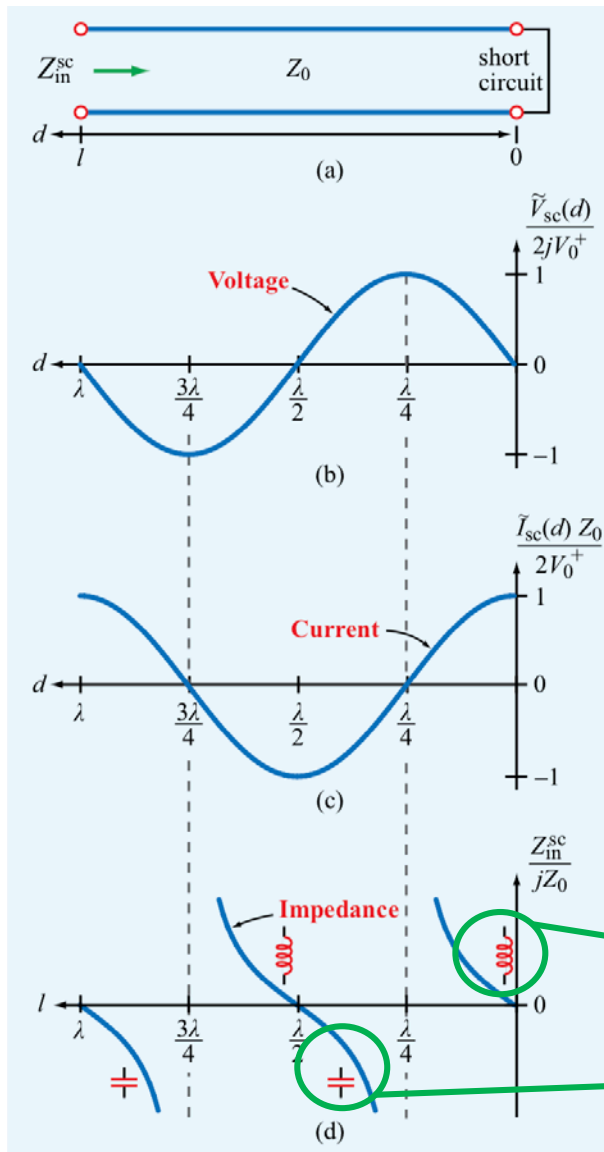
# Special cases of lossless TL: short circuit



$$Z_L = 0, \Gamma = -1, S = \infty$$


Normalized voltage amplitude

Normalized current amplitude


Normalized input impedance

$$L_{eq} = \frac{Z_0 \tan(\beta l)}{\omega} \text{ (H)}$$
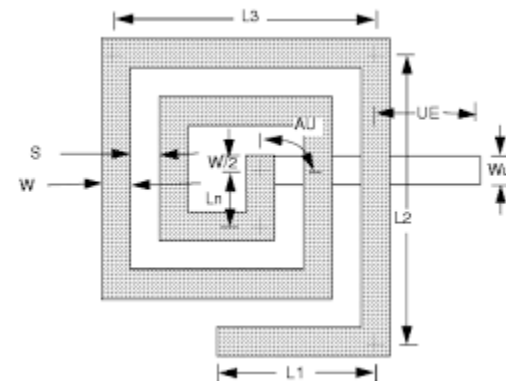
$$C_{eq} = \frac{1}{Z_0 \omega \tan(\beta l)} \text{ (F)}$$


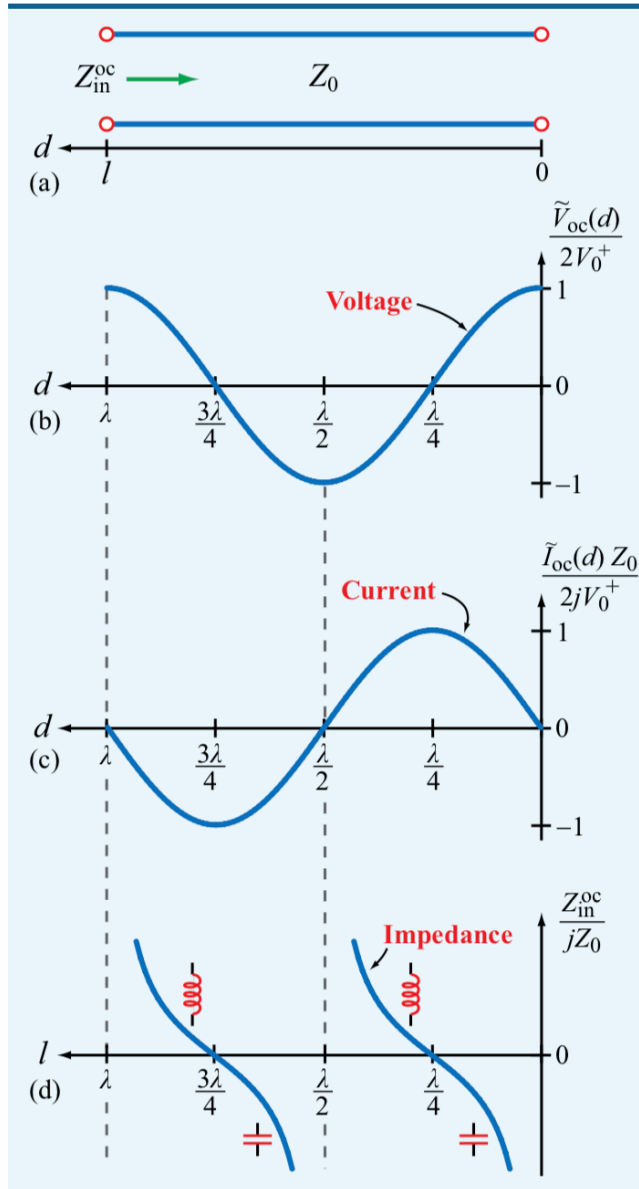
# Special cases of lossless line: open circuit



$$Z_L = \infty, \Gamma = 1, S = \infty$$

$$\tilde{V}_{oc}(d) = V_0^+ (e^{j\beta d} + e^{-j\beta d}) = 2V_0^+ \cos(\beta d)$$

$$\tilde{I}_{oc}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} - e^{-j\beta d}) = \frac{2jV_0^+}{Z_0} \sin(\beta d)$$

Normalized input impedance

$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(l)}{\tilde{I}_{oc}(l)} = -jZ_0 \cot(\beta l)$$

# Application of SC/OC Technique


Network analyzer – used to measure: impedance  
RF – at high frequencies

Measures 1)  $Z_{in}^{sc}$  and 2)  $Z_{in}^{oc} \rightarrow$  to obtain  $Z_0$  and  $\beta$

$$Z_0^2 = \underbrace{(jZ_0 \tan(\beta l))}_{Z_{in}^{sc}} \underbrace{(-jZ_0 \cot(\beta l))}_{Z_{in}^{oc}}$$

$$Z_0 = +\sqrt{Z_{in}^{sc} Z_{in}^{oc}}$$
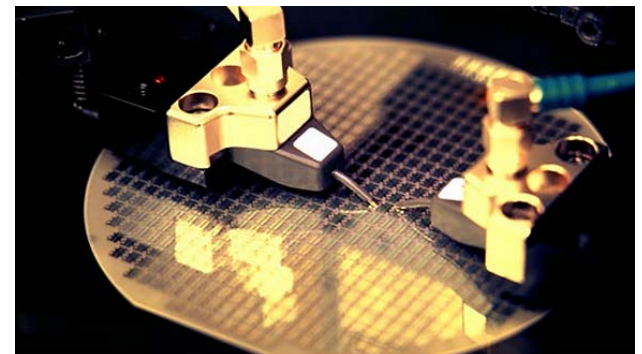
$$\tan(\beta l) = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}} \quad l \leq \lambda/2$$



## Lines of length $l = n\lambda/2$

---

$$\text{For } l = n\lambda/2, \quad (n = 1, 2, \dots) \quad \tan(\beta l) = \tan\left(\frac{2\pi n\lambda}{\lambda} \frac{1}{2}\right) = \tan(n\pi) = 0$$

$$Z_{in} = Z_0 \left( \frac{Z_L + j \tan(\beta l)}{1 + j Z_L \tan(\beta l)} \right) = Z_0 \left( \frac{Z_L}{Z_0} \right) = Z_L$$

$Z_{in} = Z_L$       Half-wavelength line **does not**  
modify load impedance

## Lines of length $l = \lambda/4$ (quarter-wave)

---

$$\text{For } l = \lambda/4 + n\lambda/2, (n = 0, 1, 2, \dots) \quad \beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

$$Z_{in} = Z_0 \left( \frac{z_L \cos(\beta l) + j \sin(\beta l)}{\cos(\beta l) + j z_L \sin(\beta l)} \right) = Z_0 \left( \frac{j}{j z_L} \right)$$


$$Z_{in} = \frac{Z_0^2}{Z_L} \quad l = \lambda/4 + n\lambda/2$$

# $\lambda/4$ transformer

---


We have a  $50\ \Omega$  lossless transmission line

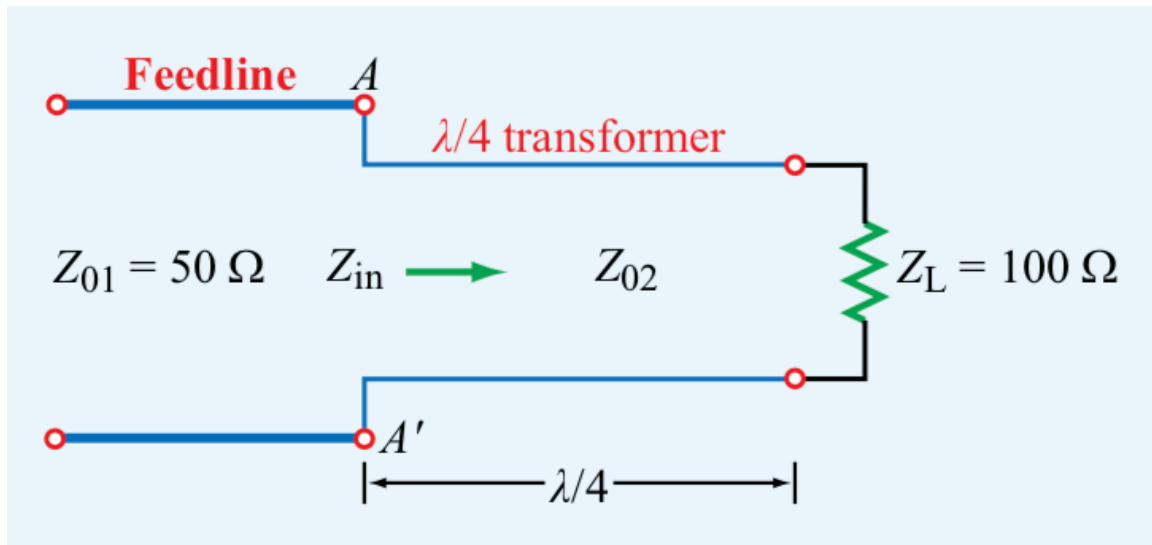We want to match to  $Z_L = 100\ \Omega$  using a quarter wave section



**Find:** required impedance of  $\lambda/4$  transformer

# $\lambda/4$ transformer

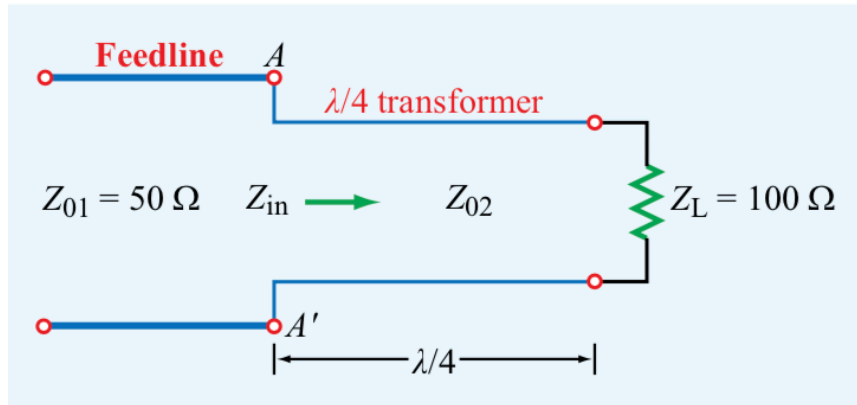

To match the feedline, need to eliminate reflections at AA'.  $\rightarrow Z_{in} = 50 \, \Omega = Z_{01}$

Quarter-wave TL:  $Z_{in} = \frac{Z_{02}^2}{Z_L}$        $Z_{02} = \sqrt{Z_{in}Z_L} = \sqrt{50 \times 100} = 70.7 \, \Omega$

Matched transmission:  $Z_L = Z_0$

- $Z_{in} = Z_0$  for all  $d$  on the line
- $\Gamma = 0$
- All incident power delivered to load