

Problem 1: Traveling Waves [30 pts]

Consider two sinusoidal waves given by the following functions:

$$E_1(z, t) = E_0 \cos(10t - 20z + \frac{\pi}{2})$$

$$E_2(z, t) = -E_0 \cos(10t + 20z + \frac{\pi}{3})$$

- a **Determine the direction of propagation and phase velocity for each of the two waves.**

Consider a single point on the wave (constant phase front), i.e.

$$\omega t - \beta z + \phi_0 = \text{const.}$$

So

$$z = \frac{1}{\beta} (\omega t + \phi_0 - \text{const.})$$

To get the propagation speed of the phase front, take the first time derivative:

$$\frac{\partial z}{\partial t} = \frac{\omega}{\beta} = u_p$$

Both ω and β of $E_1(z, t)$ are greater than zero, so the velocity is positive and thus the wave is propagating in the +z direction.

$$u_{p1} = \frac{\omega_1}{\beta_1} = \frac{10}{20} = \frac{1}{2} \text{ m/s}$$

For $E_2(z, t)$, ω is positive and β is negative, so the velocity is negative and thus the wave is propagating in the -z direction.

$$u_{p2} = \frac{\omega_2}{\beta_2} = \frac{10}{-20} = -\frac{1}{2} \text{ m/s}$$

- b **Show that both waves satisfy the wave equation, given below:**

$$\frac{\partial^2 E}{\partial z^2} - \frac{1}{u_p^2} \frac{\partial^2 E}{\partial t^2} = 0 \tag{1}$$

Plug in our expression for $E(z, t)$ and see if the equality holds.

Spatial Derivatives:

$$\begin{aligned} \frac{\partial E_1}{\partial z} &= 20E_0 \sin(10t - 20z + \frac{\pi}{2}) \quad \text{and} \quad \frac{\partial E_2}{\partial z} = 20E_0 \sin(10t + 20z + \frac{\pi}{3}) \\ \frac{\partial^2 E_1}{\partial z^2} &= -400E_0 \cos(10t - 20z + \frac{\pi}{2}) \quad \text{and} \quad \frac{\partial^2 E_2}{\partial z^2} = 400E_0 \cos(10t + 20z + \frac{\pi}{3}) \end{aligned}$$

Time Derivatives:

$$\begin{aligned}\frac{\partial E_1}{\partial t} &= -10E_0 \sin(10t - 20z + \frac{\pi}{2}) \quad \text{and} \quad \frac{\partial E_2}{\partial t} = 10E_0 \sin(10t + 20z + \frac{\pi}{3}) \\ \frac{\partial^2 E_1}{\partial t^2} &= -100E_0 \cos(10t - 20z + \frac{\pi}{2}) \quad \text{and} \quad \frac{\partial^2 E_2}{\partial t^2} = 100E_0 \cos(10t + 20z + \frac{\pi}{3})\end{aligned}$$

Substituting these results into equation 1

$$E_1 : \quad -400E_0 \cos(10t - 20z + \frac{\pi}{2}) - \frac{1}{u_{p1}^2} \left(-100E_0 \cos(10t - 20z + \frac{\pi}{2}) \right) = 0$$

$$E_2 : \quad 400E_0 \cos(10t + 20z + \frac{\pi}{3}) - \frac{1}{u_{p2}^2} \left(100E_0 \cos(10t + 20z + \frac{\pi}{3}) \right) = 0$$

We know from part a that $u_{p1} = \frac{1}{2}$ and $u_{p2} = -\frac{1}{2}$, making this substitution

$$E_1 : \quad -400E_0 \cos(10t - 20z + \frac{\pi}{2}) - 4 \left(-100E_0 \cos(10t - 20z + \frac{\pi}{2}) \right) = 0$$

$$E_2 : \quad 400E_0 \cos(10t + 20z + \frac{\pi}{3}) - 4 \left(100E_0 \cos(10t + 20z + \frac{\pi}{3}) \right) = 0$$

Thus, both $E_1(z, t)$ and $E_2(z, t)$ satisfy the wave equation!

c Find the z locations where the waves interfere constructively and destructively (where their superposition is maximal and minimal) at $t = \pi/20$ s.

First, we find the function for each wave at the specified instantaneous time:

$$E_1(z, t = \frac{\pi}{20}) = E_0 \cos(10(\frac{\pi}{20}) - 20z + \frac{\pi}{2}) = E_0 \cos(-20z + \pi)$$

$$E_2(z, t = \frac{\pi}{20}) = -E_0 \cos(10(\frac{\pi}{20}) + 20z + \frac{\pi}{3}) = -E_0 \cos(20z + \frac{5\pi}{6})$$

We can find constructive and destructive interference when $E_1 - E_2 = 0$:

$$E_0 \cos(-20z + \pi) + E_0 \cos(20z + \frac{5\pi}{6}) = 0$$

$$\cos(-20z + \pi) = -\cos(20z + \frac{5\pi}{6})$$

$$\cos(-20z + \pi) = \cos(20z + \frac{11\pi}{6})$$

Our solution for constructive interference will have the form:

$$-20z + \pi = 2\pi n + 20z + \frac{11\pi}{6}$$


$$z = \frac{\pi n}{20} - \frac{\pi}{48}$$

Our solution for destructive interference will have the form:

$$-20z + \pi = \pi(2n + 1) + 20z + \frac{11\pi}{6}$$


$$z = \frac{\pi n}{20} - \frac{11\pi}{240}$$

We can check our solution by graphing the superposition of the two waves:

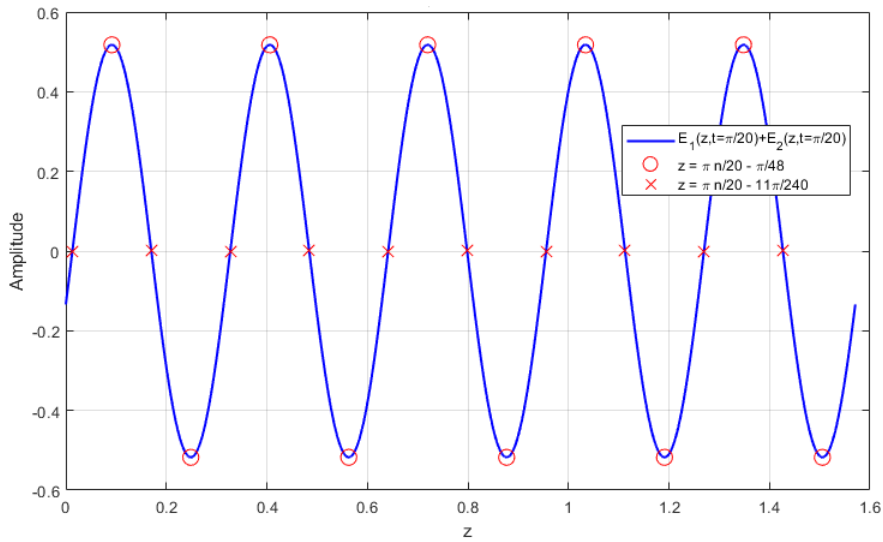

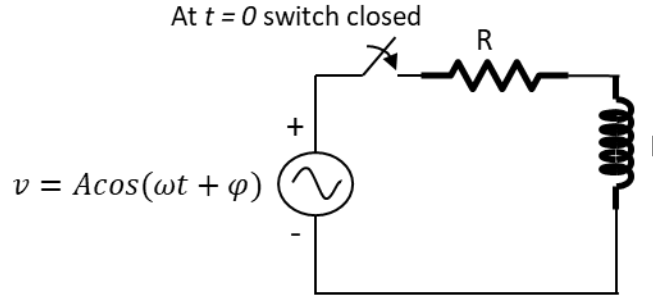Problem 2: Linear System - Time and Phasor Domain [30 pts]

Consider the simple circuit shown in the diagram below with a resistor R and an inductor L in series with a voltage source: $v(t) = A\cos(\omega t + \phi)$ and a switch. Initially the switch is open. At $t = 0$, the switch is closed.



- (a) Write the differential equation governing the behavior of the current $i(t)$ through the circuit for $t > 0$. Using KVL:

$$v_R(t) = Ri(t)$$

$$v_L(t) = L \frac{\partial i(t)}{\partial t}$$

$$v_i(t) = Ri(t) + L \frac{\partial i(t)}{\partial t}$$

- (b) Develop a solution to this differential equation in the time domain. Make an attempt toward obtaining an expression for $i(t)$ for all time. You may not be able to obtain the complete solution - please show all your work in the process.

$$v(t) = \begin{cases} \frac{\partial i}{\partial t} + \frac{R}{L}i = 0 & t \leq 0 \\ \frac{\partial i}{\partial t} + \frac{R}{L}i = \frac{A}{L}\cos(\omega t + \phi) & t > 0 \end{cases}$$

Solve for $i(t)$ when $t > 0$:

$$\begin{aligned} \frac{\partial i}{\partial t} + \frac{R}{L}i &= \frac{A}{L}\cos(\omega t + \phi) \\ e^{\frac{R}{L}t} \frac{\partial i}{\partial t} + e^{\frac{R}{L}t} \frac{R}{L}i &= e^{\frac{R}{L}t} \frac{A}{L}\cos(\omega t + \phi) \end{aligned}$$

Define $\tau = \frac{L}{R}$:

$$e^{\frac{t}{\tau}} \frac{\partial i}{\partial t} + e^{\frac{t}{\tau}} \frac{1}{\tau}i = e^{\frac{t}{\tau}} \frac{A}{L}\cos(\omega t + \phi)$$

$$\begin{aligned}\frac{\partial}{\partial t} \left(i(t) e^{\frac{t}{\tau}} \right) &= e^{\frac{t}{\tau}} \frac{A}{L} \cos(\omega t + \phi) \\ \int_0^t \frac{\partial}{\partial t} \left(i(t) e^{\frac{t}{\tau}} \right) dt &= \int_0^t e^{\frac{t}{\tau}} \frac{A}{L} \cos(\omega t + \phi) dt \\ i(t) e^{\frac{t}{\tau}} - i(0) &= \int_0^t e^{\frac{t}{\tau}} \frac{A}{L} \cos(\omega t + \phi) dt\end{aligned}$$

Substitute $i(0) = 0$:

$$i(t) = e^{\frac{-t}{\tau}} \frac{A}{L} \int_0^t e^{\frac{t}{\tau}} \cos(\omega t + \phi) dt \quad (2)$$

Solving to this point is sufficient for full credit.

Second order integration by parts:

$$\begin{aligned}\int_0^t e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) dt' &= \tau e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) \Big|_{t'=0}^{t'=t} - \tau \int_0^t e^{\frac{t'}{\tau}} (-\omega) \sin(\omega t' + \phi) dt' \\ &= \left(\tau e^{\frac{t}{\tau}} \cos(\omega t + \phi) - \tau \cos(\phi) \right) + \omega \tau \left(\tau e^{\frac{t'}{\tau}} \sin(\omega t' + \phi) \Big|_{t'=0}^{t'=t} - \omega \tau \int_0^t e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) dt' \right) \\ &= \left(\tau e^{\frac{t}{\tau}} \cos(\omega t + \phi) - \tau \cos(\phi) \right) + \omega \tau \left(\tau e^{\frac{t}{\tau}} \sin(\omega t + \phi) - \tau \sin(\phi) \right) - \omega^2 \tau^2 \int_0^t e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) dt'\end{aligned}$$

Move the last part to the left side of the equation:

$$(1 + \omega^2 \tau^2) \int_0^t e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) dt' = \tau e^{\frac{t}{\tau}} (\cos(\omega t + \phi) + \omega \tau \sin(\omega t + \phi)) - \tau (\cos(\phi) + \omega \tau \sin(\phi))$$

Define:

$$\begin{aligned}\tan(\Theta) &= \omega \tau \\ \sin(\Theta) &= \frac{\omega \tau}{\sqrt{1 + \omega^2 \tau^2}} \\ \cos(\Theta) &= \frac{1}{\sqrt{1 + \omega^2 \tau^2}}\end{aligned}$$

$$\int_0^t e^{\frac{t'}{\tau}} \cos(\omega t' + \phi) dt' = \frac{\tau}{1 + \omega^2 \tau^2} \sqrt{1 + \omega^2 \tau^2} \left(e^{\frac{t}{\tau}} \cos(\omega t + \phi - \Theta) - \cos(\phi - \Theta) \right)$$

Plug back into Eq.2:

$$i(t) = \frac{\frac{A}{L} \tau}{\sqrt{1 + \omega^2 \tau^2}} \left(\cos(\omega t + \phi - \Theta) - e^{\frac{-t}{\tau}} \cos(\phi - \Theta) \right)$$

(c) **For the same circuit and conditions, obtain the phasor expression for the current.**

$$v(t) = \text{Re}\{\tilde{V} e^{j\omega t}\} \Rightarrow \tilde{V} = A e^{j\phi}$$

$$i(t) = \text{Re}\{\tilde{I} e^{j\omega t}\}$$

$$Z_R = R, Z_L = j\omega L$$

Using KVL:

$$\tilde{V} = R\tilde{I} + j\omega L\tilde{I} = (R + j\omega L)\tilde{I}$$

- (d) **Solve this equation for the phasor current**

$$\tilde{I} = \frac{\tilde{V}}{R + j\omega L} = \frac{A}{R + j\omega L} e^{j\phi}$$

- (e) **Transform back to the time function for the current $i(t)$.**

$$i(t) = \text{Re} \left\{ \frac{A}{R + j\omega L} e^{j\phi} e^{j\omega t} \right\}, \Theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$\tilde{I} = \frac{A}{R\sqrt{1 + \omega^2 \frac{L^2}{R^2}}} e^{j\phi}$$

$$i(t) = \text{Re} \left\{ \frac{A}{R\sqrt{1 + \omega^2 \frac{L^2}{R^2}}} e^{j\phi} e^{j\omega t} \right\}$$

$$i(t) = \frac{A}{R\sqrt{1 + \omega^2 \frac{L^2}{R^2}}} \cos(\omega t + \phi - \Theta)$$

Recall that $\tau = \frac{L}{R}$:

$$i(t) = \frac{\frac{A}{L}\tau}{\sqrt{1 + \omega^2 \tau^2}} \cos(\omega t + \phi - \Theta)$$


- (f) **Comment on the methodology of the time domain versus using the phasor domain to obtain the solution to this linear system.**

The first term of the expression found in part b is the same as the solution found in part e. This term is the steady state solution, the solution as $t \rightarrow \tau$. The second term in the expression for part b is the transient solution, which has no t dependence. When we only care about the steady state solution, phasor domain solutions are far easier to work through.

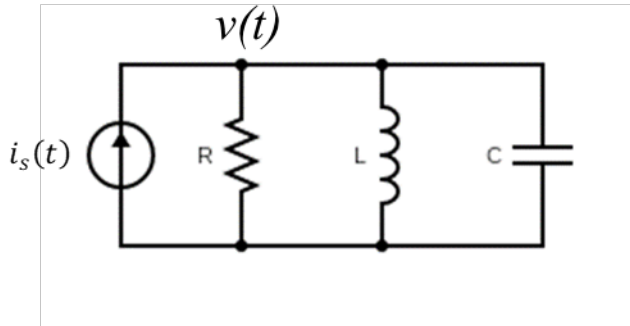Problem 3: Circuit Analysis using the Phasor Domain [40 pts]

Consider a parallel RLC circuit shown in the figure below and driven by the current source:

$$i_s(t) = I_0 \cos(\omega t + \frac{\pi}{3}) [\text{A}]$$



- (a) Obtain the equation for $v(t)$ in terms of R, L, C , and $i_s(t)$.

Using KCL:

$$i_s(t) = i_C(t) + i_R(t) + i_L(t)$$

$$i_s(t) = C \frac{\partial v(t)}{\partial t} + \frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t') dt'$$

- (b) Convert this differential equation to the phasor domain.

$$\tilde{I}_s = j\omega C \tilde{V} + \frac{1}{R} \tilde{V} + \frac{1}{j\omega L} \tilde{V} = \tilde{V} \left(j\omega C + \frac{1}{R} + \frac{1}{j\omega L} \right)$$

where $\tilde{I}_s = I_0 e^{j\frac{\pi}{3}}$

- (c) Solve the equation for \tilde{V} , the steady-state phasor voltage across each component.

$$\tilde{V} = \frac{\tilde{I}_s}{j\omega C + \frac{1}{R} + \frac{1}{j\omega L}} = \frac{j\omega RL}{R - \omega^2 RLC + j\omega L} \tilde{I}_s$$

- (d) Using the phasor domain analysis obtain the full time domain expression $v(t)$.

$$\tilde{V} = \frac{j\omega RL}{R - \omega^2 RLC + j\omega L} \tilde{I}_s$$

$$\tilde{V} = \frac{\omega R L e^{j\frac{\pi}{2}}}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2} e^{j\theta}} \tilde{I}_s$$

where

$$\theta = \tan^{-1} \left(\frac{\omega L}{R - \omega^2 RLC} \right)$$

$$\tilde{V} = \frac{\omega RL}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2}} e^{j(\frac{\pi}{2} - \theta)} \tilde{I}_s$$

$$v(t) = \frac{\omega RLI_0}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2}} \cos(\omega t + \frac{\pi}{3} - \Theta)$$

where $\Theta = \frac{\pi}{2} - \theta$