


ELEN 3401 Electromagnetics Problem Set #3

DUE: Friday Feb. 21

Please include your name and UNI on the assignment

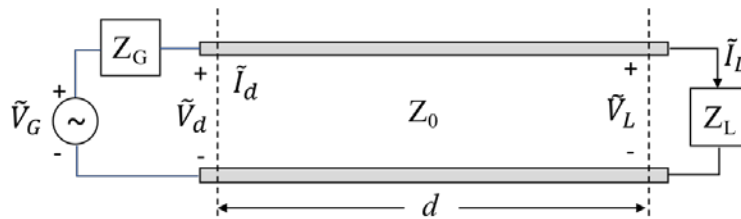Problem 1: Voltage and Current along Transmission Line

A lossless transmission line of characteristic impedance $Z_0 = 50 \, \Omega$ and length $d = 17 \, \text{m}$ is connected to an unknown load Z_L and to a generator $\tilde{V}_G = 10\angle 0^\circ$ volts as shown in the figure below. The internal impedance Z_G , of the generator is unknown. The signal wavelength on the line is $\lambda = 8 \, \text{m}$. The current and voltage on the line at the generator end are measured and found to be $\tilde{I}_d = 40\angle 0^\circ \, \text{mA}$ and $\tilde{V}_d = 6\angle 0^\circ$ volts.



- Determine the wave impedance Z_d at the generator end, as well as the generator's internal impedance Z_G .
- Determine the load impedance Z_L .

Problem 2: Standing Wave Ratio

Consider a lossless transmission line with a characteristic impedance of $100\text{-}\Omega$ that is terminated with an unknown load impedance. The line is operated at a frequency corresponding to a wavelength $\lambda = 40 \, \text{cm}$. The standing wave ratio along this line is measured to be $S = 3$. The distance from the load to the first voltage minimum is measured to be $5 \, \text{cm}$.

Based on these two measurements, determine the unknown load impedance.

Problem 3: Power Flow in Lossless Transmission Line

An antenna with a load impedance: $Z_L = (75 + j25) \, \Omega$ is connected to a transmitter through a 50Ω lossless transmission line. If under matched conditions the transmitter can deliver 46W to the load, obtain the power that can be delivered to the antenna. Assume that $Z_g = Z_0$.

Problem 4: Transients on Transmission Lines

We have a 1 m long lossless line characterized by $Z_0 = 50 \, \Omega$ and $u_p = 2c/3$ (where c is the velocity of light). The line is fed by a step voltage applied at $t = 0$ by a generator circuit with $V_g = 60 \, \text{V}$ and $R_g = 100 \, \Omega$. The line is terminated in a load with $R_L = 25 \, \Omega$.

- a) Generate a bounce diagram for the voltage $V(z, t)$ on this line.
- b) Use the bounce diagram to plot $V(t)$ at a point midway (50 cm) along the length of the line from $t = 0$ to $t = 25 \, \text{ns}$.
- c) Find the steady-state voltage on the line.